

COEN-2710 Microprocessors - Lecture 6

Arithmetic for Computers – Building the ALU

(Ch.3 + Appendices A,C)

Cristinel Ababei

Marquette University

Department of Electrical and Computer Engineering

1

Outline

- ❖ Basics
- ❖ ALU
- ❖ Carry look ahead
- ❖ Shifting

2

2

Design process summary

- ❖ 1. Divide and Conquer:
 - ◆ Outline what needs to be accomplished
 - ◆ Formulate solution in terms of simpler components
 - ◆ Design each component
- ❖ 2. Connect, test, and verify:
 - ◆ Put together the basic building blocks
 - ◆ Verify that every possible input gives valid output
- ❖ 3. Successive refinement:
 - ◆ Evaluate results, correct errors, improve design

3

3

Design Methodologies

- ❖ Hierarchical Design to manage complexity
- ❖ Top Down vs. **Bottom Up**
 - ◆ Block Diagrams
 - ◆ Decomposition into Bit Slices
 - ◆ Truth Tables, K-Maps
 - ◆ Circuit Diagrams
 - ◆ Other: state & timing diagrams, ...
- ❖ Measurement Criteria:
 - ◆ Design Performance
 - ◆ Design Cost
 - ◆ Design Time
 - ◆ Gate count
 - ◆ Power dissipation
 - ◆ ...

4

4

First step: arithmetic circuits

Questions to be addressed:

- ❖ How do we represent numbers?
 - ◆ Integers vs. floating-point (i.e., real numbers)
 - ◆ Negative numbers
- ❖ How do we implement:
 - ◆ Addition?
 - ◆ Subtraction?
 - ◆ Multiplication?
 - ◆ Division?
- ❖ How do we handle errors? (overflow, etc.)

5

5

Possible Representations

Sign Magnitude:	One's Complement	Two's Complement
000 = +0	000 = +0	000 = +0
001 = +1	001 = +1	001 = +1
010 = +2	010 = +2	010 = +2
011 = +3	011 = +3	011 = +3
100 = -0	100 = -3	100 = -4
101 = -1	101 = -2	101 = -3
110 = -2	110 = -1	110 = -2
111 = -3	111 = -0	111 = -1

- ❖ Issues: balance, number of zeros, ease of operations
- ❖ Which one is best? Why?

6

6

RISC-V - Two's complement

- ❖ Positive numbers - regular binary
- ❖ Negative numbers
 - ◆ Take equivalent positive binary number
 - ◆ Flip the bits
 - ◆ Add 1
- ❖ Significant design advantages
 - ◆ Easy to negate numbers (steps given above)
 - ◆ Easy to check positive/negative (still have sign bit)
 - ◆ Biggest one: adding and subtracting work right!

7

7

Sign extension

We will often need to take a 16-bit number and put it into a 32-bit (or 64-bit) location.

Doing this in two's complement requires some slight additional care:

- ◆ Must always replicate the left-most bit (sign bit) into the other positions.
- ◆ This process is called **sign-extension**, and is built into most commands

8

8

Unsigned numbers

- ❖ Sometimes we have variables (like counters) that can only be positive. By **not** using two's complement for these cases, we get a whole extra bit of representation.
- ❖ Positive-only numbers are called ***unsigned***.
- ❖ Math commands on unsigned numbers will have to be handled carefully, both in design and in programming (especially with the built-in sign extension)

9

9

Addition & Subtraction

- ❖ Two's complement operations easy
 - ◆ subtraction using addition of negative numbers
- ❖ Overflow (result too large for finite computer word):

$$\begin{array}{r} 0111 \\ + 1010 \\ \hline \end{array}$$

- ◆ e.g., adding two n-bit numbers does not yield an n-bit number


$$\begin{array}{r} 0111 \\ + 0001 \\ \hline 1000 \end{array}$$

10

10

Integer Addition

❖ Example: 7 + 6

 

- Overflow if result out of range
 - Adding **positive** and **negative** operands, no overflow
 - Adding **two positive** operands
 - Overflow if result sign is 1
 - Adding **two negative** operands
 - Overflow if result sign is 0

11

11

Integer Subtraction

❖ Add negation of second operand

❖ Example: 7 - 6 = 7 + (-6)

$$\begin{array}{r}
 +7: \quad 0000\ 0000 \dots 0000\ 0111 \\
 -6: \quad 1111\ 1111 \dots 1111\ 1010 \\
 \hline
 +1: \quad 0000\ 0000 \dots 0000\ 0001
 \end{array}$$

❖ Overflow if result out of range

- ◆ Subtracting two **positive** or two **negative** operands, no overflow
- ◆ Subtracting **positive** from **negative** operand
 - Overflow if result sign is 0
- ◆ Subtracting **negative** from **positive** operand
 - Overflow if result sign is 1

12

12

Practice

1. Represent +14, -14, +25, and -25 in 6-bit two's complement notation
2. Using these representations,
 - a) Add -14 + -14
 - b) Add 14 + -25
 - c) Add 14 + 25
3. Any overflows?

13

13

Detecting Overflow

- ❖ No overflow when adding a positive and a negative number
- ❖ No overflow when signs are the same for subtraction
- ❖ Overflow occurs when the value affects the sign:
 - ◆ adding two positives yields a negative
 - ◆ adding two negatives gives a positive
 - ◆ subtract a negative from a positive and get a negative
 - ◆ subtract a positive from a negative and get a positive
- ❖ How to handle overflow:
 - ◆ Control jumps to predefined address for exception
 - ◆ Interrupted address is saved for possible resumption
 - ◆ Ignore it (several commands for unsigned arithmetic do not cause exceptions on overflow)

14

14

Outline

- ❖ Basics
- ❖ **ALU**
- ❖ Carry look ahead
- ❖ Shifting

15

15

The Arithmetic Logic Unit (ALU)

- ❖ Will use a bottom-up approach to design a **32-bit** ALU (64-bit is similar)
- ❖ Based on the chosen instruction set, we need to be able to implement:

- ◆ Addition
- ◆ Subtraction
- ◆ Bit-wise AND
- ◆ Bit-wise OR
- ◆ Set on less-than
- ◆ Zero-flag (BNE)
- ◆ Nor



Will be integrated into ALU

- ◆ Shift left
- ◆ Shift right
- ◆ Multiplication
- ◆ Division



(Will do later)

16

16

Building blocks: Start with 1-bit ALU

Start with just AND, OR, ADD functions

ALU inputs:

- ◆ Input A, Input B, Carry In, Control flags
(for deciding what operation is implemented)

ALU outputs:

- ◆ Result, Carry Out

- ❖ *Practice*: Work out the logic formulas for Add from the basic concept of addition

17

17

ALU formulas

AND

- ◆ Result = AB

OR

- ◆ Result = $A+B$

ADD


- ◆ Result = $\bar{A}\bar{B}C_i + A\bar{B}\bar{C}_i + \bar{A}B\bar{C}_i + ABC_i$
- ◆ Carry Out = $AB + AC_i + BC_i$

18

18

First-pass ALU Implementation

 - ❖ Implement AND, OR, ADD logic
- ❖ Use 3-input mux to select output function (Operation)




19

19

Extending to full 32-bit ALU

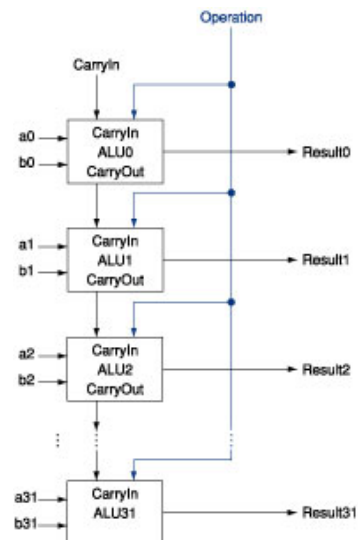- ❖ Just need to hook up in series (in chain) so the carries will propagate.
- ❖ This is an example of hierarchical design (using building blocks) - what the book calls “abstraction”




20

20

Including subtraction

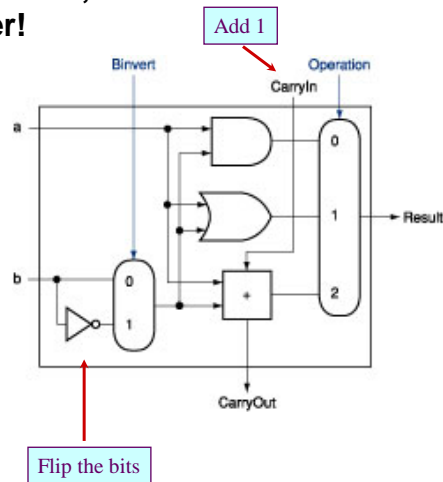- ❖ Subtraction is just A plus \bar{B} , so just need an inverter!
- ❖ Implement AND, OR, ADD logic
- ❖ Use 2-input mux to choose ADD/SUB (Binvert)
- ❖ Use 3-input mux to select output function (Operation)




21

21

Including NOR

- ❖ A NOR operation can be written as $\bar{A} \bullet \bar{B}$. Therefore, we can use the AND gate. Just need another inverter!
- ❖ To implement NOR, set

Ainvert and
Binvert and
Operation = AND

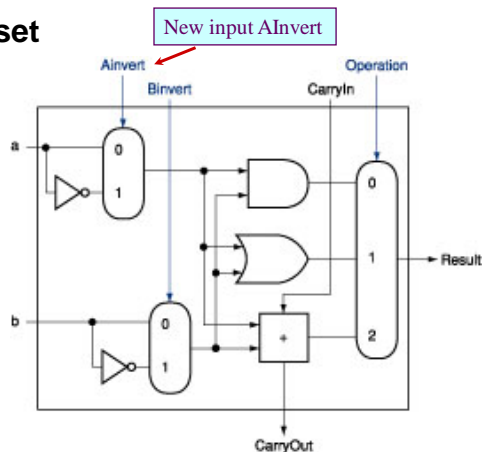

22

22

Including Set on Less Than (SLT)

- ❖ SLT sets output = 1 if $A < B$, 0 else
- ❖ Bitwise formula for slt:
 - Result = 0, unless $A-B < 0$ and this is LSB
- ❖ So:
 - ◆ Set Binvert (to perform A-B)
 - ◆ Add a new input called Less
 - Connect to logical 0, for all bits except LSB
 - Connect LSB Less input to sign bit (MSB) from A-B
 - ◆ Question: Where do we get that sign bit? (We will be setting the result output of the MSB to logic 0)
 - ◆ Answer: Need slightly modified ALU for MSB; add an output called Set connected to MSB adder

23

23



Final Standard and MSB Units

Standard 1-bit units
Chain 31 of them (for bits
Index 0..30)

LSB: Connect to Set
Else: Hardwire to 0

MSB unit
Use for last bit
(bit Index 31)

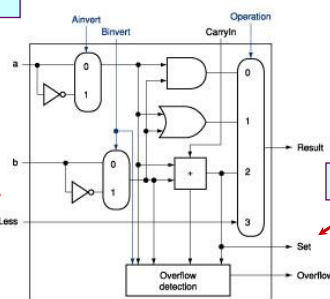 (Note we've also added overflow
detection to the MSB.)



MSB sign bit

24


24

Final Version with Zero-check flag

Control lines: "ALU operation", 4 bits:

- ❖ Ainvert
- ❖ Bnegate
- ❖ Operation1
- ❖ Operation0

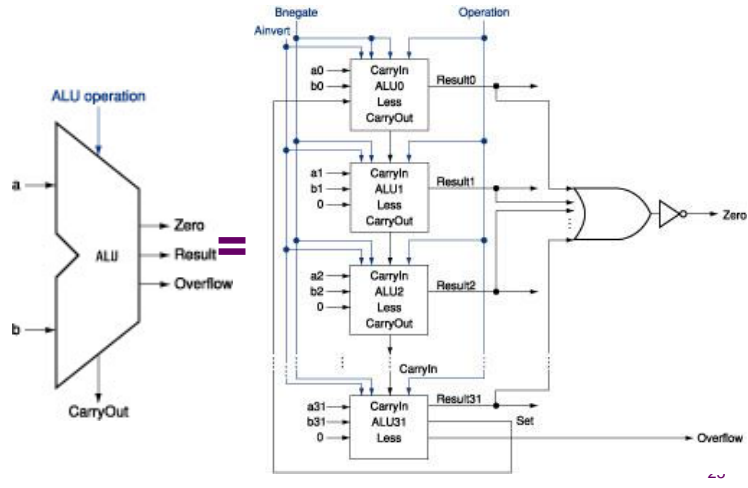0000 = and
 0001 = or
 0010 = add
 0110 = sub
 0111 = slt
 1100 = NOR



25

Problem for You

- ❖ Analyze the performance of this design
 - ◆ Does it implement the required tasks? YES
 - ◆ How long does it take to do it?
 - Assume: The logic in a 1-bit adder takes 2 levels of logic to produce the carry output, and each gate has a 1 ns delay in this particular design.
 - What's the total amount of delay from IN to OUT for a 32-bit ALU to do an ADD?
- ❖ This design is called a **ripple carry adder**.
Not the best
- ❖ What is the minimum delay possible?

26

26

Outline

- ❖ Basics
- ❖ ALU
- ❖ Carry look ahead
- ❖ Shifting

27

27

Carry look-ahead

So, what do we know without any delay?

- ◆ The values of the a_i and b_i inputs

What can we do with them?

- ◆ Figure out when a Carry Out will be *generated* (regardless of the Carry In value).

$$g_i = a_i b_i$$

- ◆ Figure out when a Carry In will be *propagated* to the Carry Out. (when c_{out} will equal c_{in})

$$p_i = a_i + b_i$$

- ❖ At each bit, we get $c_{out} = g + p c_{in}$

28

28

4-bit case, expanded

$$c_1 = g_0 + p_0 c_0$$

$$\begin{aligned} c_2 &= g_1 + p_1 c_1 \\ &= g_1 + p_1 (g_0 + p_0 c_0) \\ &= g_1 + p_1 g_0 + p_1 p_0 c_0 \end{aligned}$$

$$\begin{aligned} c_3 &= g_2 + p_2 c_2 \\ &= g_2 + p_2 (g_1 + p_1 g_0 + p_1 p_0 c_0) \\ &= g_2 + p_2 g_1 + p_2 p_1 g_0 + p_2 p_1 p_0 c_0 \end{aligned}$$

$$\begin{aligned} c_4 &= g_3 + p_3 c_3 \\ &= g_3 + p_3 (g_2 + p_2 g_1 + p_2 p_1 g_0 + p_2 p_1 p_0 c_0) \\ &= g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0 + p_3 p_2 p_1 p_0 c_0 \end{aligned}$$

29

29

❖ Can we build a 16-bit adder this way?

- ◆ How much delay would it have?
- ◆ How many gate inputs for the MSB Carry Out?

❖ How about a compromise?

Hierarchical design approach:

- ◆ Put together 4 4-bit carry-lookahead adders
- ◆ Create 4-bit signals: propagates (P0-3), generates (G0-3), carries (C1- 4). Example formulas:

$$P_0 = p_3 p_2 p_1 p_0$$

$$G_0 = g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0$$

$$C_1 = G_0 + P_0 c_0$$

30


30

16-bit hierarchical carry-lookahead

❖ How much total delay is there in this design?

- ◆ 1st level p & g in
(a & b in → p & g out)
- ◆ 1st level P & G out?
(p & g in → P & G out)
- ◆ 2nd level Carry Out?
(P & G in → C out)
- ◆ 1st level carry in?
(C in + p & g in → c in)
- ◆ Result out?
(a & b & c in → Result out)

❖ What is the performance improvement?

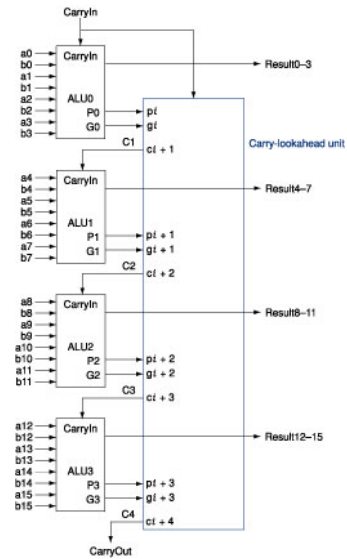

31

31

Outline

- ❖ Basics
- ❖ ALU
- ❖ Carry look ahead
- ❖ Shifting

32

32

Shifting

Shifting we need to implement (6 kinds)

- ◆ **Direction: Left or right**
- ◆ **Extension:**
 - Logical (Zero extended)
 - Arithmetic (Sign extended)
 - Rotate (extended by rotation of bits)

❖ **Goal – shift in 1 clock cycle. Common types:**


- Barrel Shifter (Full mux into flip-flop for each bit)
- Combinational Shifter (Hierarchical, MUX-based)
- Funnel Shifter (Selects a region of a doubled register)

33

33

Combinational Shifter from MUXes

❖ 8-bit right shifter

 

Issues/questions


- ❖ What comes in the MSBs?
- ❖ How many levels for 32-bit shifter?
- ❖ How can we do rotates (circular shifting)?

34

34

Funnel Shifter

 - ❖ Advantage: Can do all 6 kinds of shifts with same hardware (can still use combinational mux design).



Type	Left half	Right half	Offset
Logical Left	$R_{N-1} - R_0$	$0 \dots 0$	$N-k$
Logical Right	$0 \dots 0$	$R_{N-1} - R_0$	k
Arithmetic Left	$R_{N-1} - R_0$	$0 \dots 0$	$N-k$
Arithmetic Right	$R_{N-1} \dots R_{N-1}$	$R_{N-1} - R_0$	k
Rotate Left	$R_{N-1} - R_0$	$R_{N-1} - R_0$	$N-k$
Rotate Right	$R_{N-1} - R_0$	$R_{N-1} - R_0$	k