

 


Edge detection circuit



 


Finite State Machines (FSM) in VHDL

 Sequential circuits are modeled on FSM's because they transit among a finite number of internal states.



   Example of Mealy machine: Edge detector of rising edges



VHDL Description: "Two process model"

(2)

```
library ieee;  
use ieee.std_logic-1164.all;
```

```
entity edge_detect is  
  port ( clk, reset, level : in std_logic;  
         tick : out std_logic);  
end edge_detect;
```

```
architecture MEALY_ARCH of edge_detect is
```

```
  type state-type ( S0, S1 );  
  signal state-current, state-next : state-type;
```

```
  begin
```

```
    -- state register; process #1
```

```
    process (clk, reset)  
    begin
```

```
      if (reset = '1') then
```

```
        state-current <= S0;
```

```
      elsif (clk'event and clk = '1') then
```

```
        state-current <= state-next;
```

```
      end if;
```

```
    end process;
```

```
    -- next state and output logic; process #2
```

```
    process (state-current, level)
```

```
    begin
```

```
      state-next <= state-current;
```

```
      tick <= '0';
```

```
      case state-current is
```

```
        when S0 =>
```

```
          if level = '1' then
```

```
            state-next <= S1;
```

```
            tick <= '1';
```

```
          end if;
```

```
        when S1 =>
```

```
          if level = '0' then
```

```
            state-next <= S0;
```

```
          end if;
```

```
      end case;
```

```
    end process;
```

```
  end MEALY_ARCH;
```

"imagine"
them being
executed
concurrently.

describes how
states are
transitioned
from one to
another.