

# EE-379 Embedded Systems and Applications

---

## Computer Basics

Cristinel Ababei  
Department of Electrical Engineering, University at Buffalo  
Spring 2013

*Note: This course is offered as EE 459/500 in Spring 2013*

## Overview


---

- Part 1 – Datapaths
  - Introduction
  - Datapath Example
    - Arithmetic Logic Unit (ALU)
    - Shifter
  - Datapath Representation and Control Word
  
- Part 2 – A Simple Computer
  - Instruction Set Architecture (ISA)
  - Single-Cycle Hardwired Control
  
- Part 3 – Pipelining
  - Single-Cycle Computer Issues
  - Pipelining concept
  - Pipelined design of Simple Computer
 
## Introduction

---


- Computer Specification
  - **Instruction Set Architecture (ISA)** - the specification of a computer's appearance to a programmer at its lowest level
  - **Computer Architecture** - a high-level description of the hardware implementing the computer derived from the ISA
  - The architecture usually includes additional specifications such as speed/performance, cost, and reliability


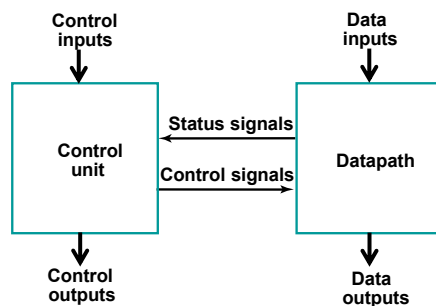
## Introduction


---

- Simple computer architecture decomposed into:
  - **Datapath**: performing operations (i.e., data manipulation)
    - A set of registers
    - Microoperations performed on the data stored in the registers
    - A control interface
  - **Control unit**: controlling datapath operations
    - Programmable & Non-programmable


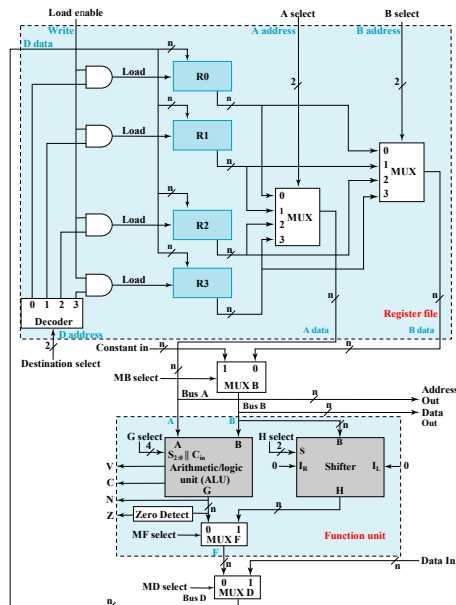
## Datapath Example


- Register file:
  - Four parallel-load regs
  - Two mux-based register selectors
  - Register destination decoder
- Microoperation implementation
  - Mux B for external constant input
  - Bus A and B with external address and data outputs
  - Function Unit:
    - ALU and Shifter with Mux F for output select
    - Mux D for external data input
    - Logic for generating status bits: V, C, N, Z


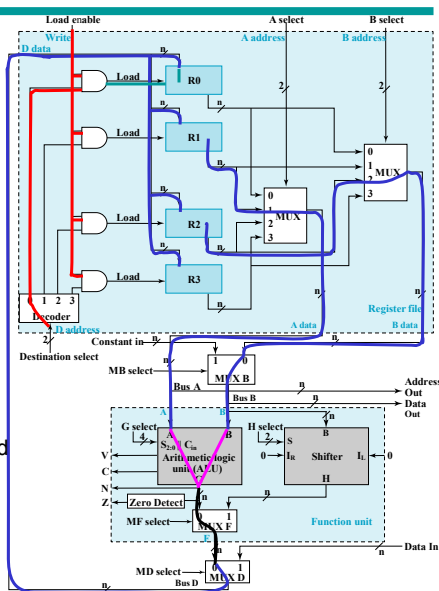
## Datapath Example: Performing a Microoperation

Microoperation:  $R0 \leftarrow R1 + R2$


- Apply 01 to A select to place contents of R1 onto Bus A
- Apply 10 to B select to place contents of R2 onto B data and apply 0 to MB select to place B data on Bus B
- Apply 0010 to G select to perform addition  $G = \text{Bus A} + \text{Bus B}$
- Apply 0 to MF select and 0 to MD select to place the value of G onto BUS D
- Apply 00 to Destination select to enable the Load input to R0
- Apply 1 to Load Enable to force the Load input to R0 to 1 so that R0 is loaded on the clock pulse (not shown)
- The overall microoperation requires 1 clock cycle


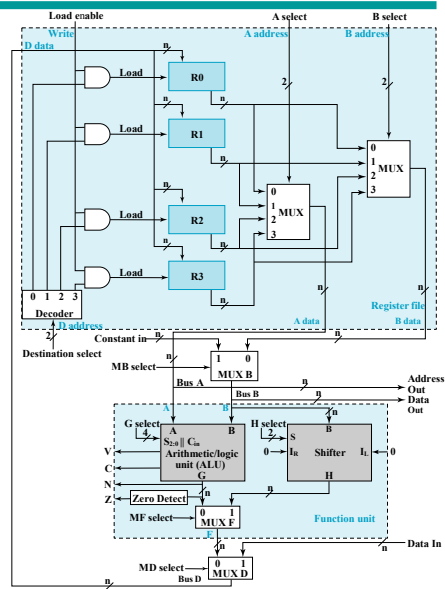
## Datapath Example: Key Control Actions for Microoperation Alternatives

Various microoperations:

- Perform a shift microoperation:  
apply 1 to MF select
- Use a constant in a micro-operation using Bus B: apply 1 to MB select
- Provide an address and data for a memory or output write microoperation – apply 0 to Load enable to prevent register loading
- Provide an address and obtain data for a memory or output read microoperation – apply 1 to MD select
- For some of the above, other control signals become don't cares




## Overview

- Part 1 – Datapaths
  - Introduction
  - Datapath Example
    - Arithmetic Logic Unit (ALU)
    - Shifter
  - Datapath Representation and Control Word
- Part 2 – A Simple Computer
  - Instruction Set Architecture (ISA)
  - Single-Cycle Hardwired Control
- Part 3 – Pipelining
  - Single-Cycle Computer Issues
  - Pipelining concept
  - Pipelined design of Simple Computer
 
# Arithmetic Logic Unit (ALU)


- Decompose the ALU into:
  - An arithmetic circuit & A logic circuit
  - A selector to pick between the two circuits



# Arithmetic Circuit


- Arithmetic circuit design
  - Decompose the arithmetic circuit into:
    - An n-bit parallel adder
    - A logic block that selects four choices for input B to the adder
- There are only four functions of B to select as Y in  $G = A + Y + C_{in}$ :

Y	$C_{in} = 0$	$C_{in} = 1$
0	$G = A$	$G = A + 1$
B	$G = A + B$	$G = A + \overline{B} + 1$
$\overline{B}$	$G = A + \overline{B}$	$G = A + B + 1$
1	$G = A - 1$	$G = A$

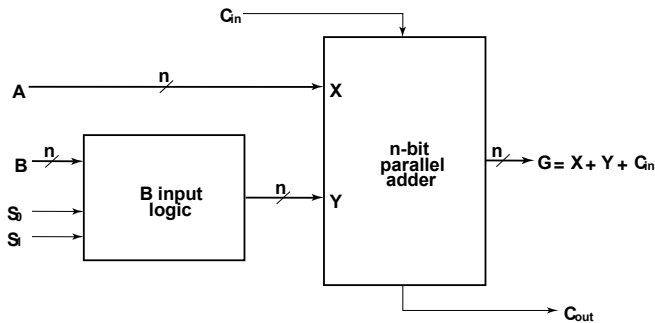


Arithmetic operations

## 4-Bit Basic Left/Right Shifter

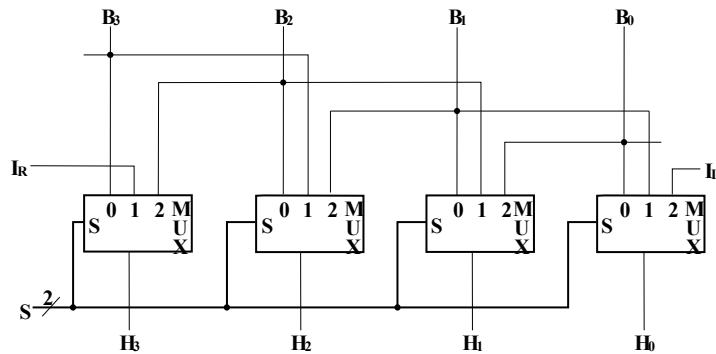

- Serial Inputs:
  - $I_R$  for right shift
  - $I_L$  for left shift
- Shift Functions:
  - $(S_1, S_0) = 00$  Pass B unchanged
  - 01 Right shift
  - 10 Left shift
  - 11 Unused


## Barrel Shifter

 

- A rotate is a shift in which the bits shifted out are inserted into the positions vacated
- The circuit rotates its contents left from 0 to 3 positions depending on S:
  - S = 00 position unchanged
  - S = 01 rotate left by 1 positions
  - S = 10 rotate left by 2 positions
  - S = 11 rotate left by 3 positions

## Combinational Shifter from MUXes


Basic Building Block

 

• Example 8-bit:

- Layer 1 shifts by 0, 4
- Layer 2 shifts by 0, 2
- Layer 3 shifts by 0, 1

8-bit right shifter

 


- Large barrel shifters can be constructed using:
  - Layers of multiplexers
  - 2-dimensional array circuits designed at the electronic level

## Overview


- Part 1 – Datapaths
  - Introduction
  - Datapath Example
    - Arithmetic Logic Unit (ALU)
    - Shifter
  - Datapath Representation and Control Word
- Part 2 – A Simple Computer
  - Instruction Set Architecture (ISA)
  - Single-Cycle Hardwired Control
- Part 3 – Multiple Cycle Hardwired Control
  - Single Cycle Computer Issues
  - Sequential Control Design
 
# Datapath Representation

- In the register file:
  - Select inputs for multiplexers => A address & B address
  - Decoder input => D address
  - Load enable => write
  - Input data to the registers => D data
  - Multiplexer outputs => A data & B data
- The register file now appears like a memory based on clocked flip-flops
- FS?


 
## Definition of Function Select (FS) Codes



FS(3:0)	MF Select	G Select(3:0)	H Select(1:0)	Microoperation
0000	0	0000	XX	$F \leftarrow 1$
0001	0	0001	XX	$F \leftarrow + 1$
0010	0	0010	XX	$F \leftarrow + B$
0011	0	0011	XX	$F \leftarrow + 3 + 1$
0100	0	0100	XX	$F \leftarrow + \bar{B}$
0101	0	0101	XX	$F \leftarrow + \bar{3} + 1$
0110	0	0110	XX	$F \leftarrow - 1$
0111	0	0111	XX	$F \leftarrow$
1000	0	1X00	XX	$F \leftarrow \wedge 3$
1001	0	1X01	XX	$F \leftarrow \vee 3$
1010	0	1X10	XX	$F \leftarrow \oplus 3$
1011	0	1X11	XX	$F \leftarrow \ominus 3$
1100	1	XXXX	00	$F \leftarrow$
1101	1	XXXX	01	$F \leftarrow B$
1110	1	XXXX	10	$F \leftarrow \bar{B}$

Boolean Equations:

$$MF_i = F_3 F_2$$

$$G_i = F_i$$

$$H_i = F_i$$



## The Control Word

- The datapath has many control input signals, can be organized into a **control word**
- To execute a microinstruction, we apply control word values for a clock cycle

15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
DA		AA		BA		M B		FS			M D		R W		


Control word

DA – D Address, AA – A Address

BA – B Address, MB – Mux B

FS – Function Select, MD – Mux D

RW – Register Write

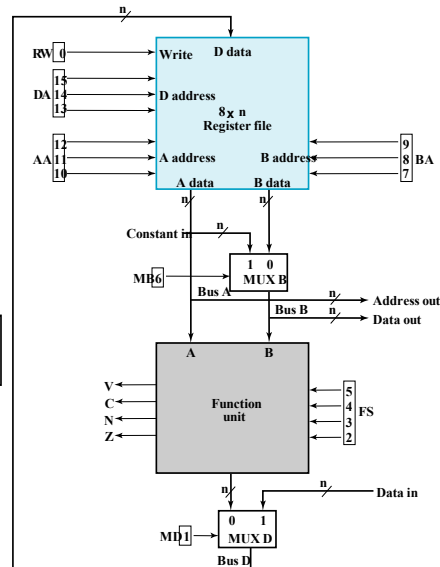

## Control Word Encoding

DA, AA, BA		MB		FS		MD		RW	
Function	Code	Function	Code	Function	Code	Function	Code	Function	Code
R0	000	Register	0	$F \leftarrow$	0000	Function	0	No write	0
R1	001	Constant	1	$F \leftarrow + 1$	0001	Data In	1	Write	1
R2	010			$F \leftarrow + B$	0010				
R3	011			$F \leftarrow + B + 1$	0011				
R4	100			$F \leftarrow + \bar{B}$	0100				
R5	101			$F \leftarrow + \bar{B} + 1$	0101				
R6	110			$F \leftarrow - 1$	0110				
R7	111			$F \leftarrow$	0111				
				$F \leftarrow \wedge$	1000				
				$F \leftarrow \vee$	1001				
				$F \leftarrow \oplus$	1010				
				$F \leftarrow \ominus$	1011				
				$F \leftarrow B$	1100				
				$F \leftarrow \bar{B}$	1101				
				$F \leftarrow B$	1110				
				$F \leftarrow \bar{B}$	1111				


## Microoperations for the Datapath – Symbolic & Binary Representation

Micro-operation	DA	AA	BA	MB	FS	MD	RW
$R1 \leftarrow 2 - R3$	R1	R2	R3	Register	$F = A + \bar{B} + 1$	Function	Write
$R4 \leftarrow R6$	R4	—	R6	Register	$F = s1 B$	Function	Write
$R7 \leftarrow 7 + 1$	R7	R7	—	Register	$F = A + 1$	Function	Write
$R1 \leftarrow 0 + 2$	R1	R0	—	Constant	$F = A + B$	Function	Write
Data out $\leftarrow 3$	—	—	R3	Register	—	—	No Write
$R4 \leftarrow \text{ata in}$	R4	—	—	—	—	Data in	Write
$R5 \leftarrow$	R5	R0	R0	Register	$F = A \oplus$	Function	Write

Micro-operation	DA	AA	BA	MB	FS	MD	RW
$R1 \leftarrow 2 - R3$	001	010	011	0	0101	0	1
$R4 \leftarrow R6$	100	XXX	110	0	1110	0	1
$R7 \leftarrow 7 + 1$	111	111	XXX	0	0001	0	1
$R1 \leftarrow 0 + 2$	001	000	XXX	1	0010	0	1
Data out $\leftarrow 3$	XXX	XXX	011	0	XXXX	X	0
$R4 \leftarrow \text{ata in}$	100	XXX	XXX	X	XXXX	1	1
$R5 \leftarrow$	101	000	000	0	1010	0	1

## Datapath Simulation

 

## Overview

---

- Part 1 – Datapaths
  - Introduction
  - Datapath Example
    - Arithmetic Logic Unit (ALU)
    - Shifter
  - Datapath Representation and Control Word
- Part 2 – A Simple Computer
  - **Instruction Set Architecture (ISA)**
  - Single-Cycle Hardwired Control
- Part 3 – Pipelining
  - Single-Cycle Computer Issues
  - Pipelining concept
  - Pipelined design of Simple Computer

## Instruction Set Architecture (ISA) for Simple Computer (SC)

---

- **Instructions** are stored in RAM or ROM as a *program*, the addresses for instructions are provided by a *program counter (PC)*
  - Count up or load a new address
  - The PC and associated control logic are part of the Control Unit
- A typical instruction specifies:
  - Operands to use
  - Operation to be performed
  - Where to place the result, or which instruction to execute next
- Executing an instruction
  - Activate the necessary sequence of operations specified by the instruction
  - Be controlled by the control unit and performed in:
    - Datapath
    - Control unit
    - External hardware such as memory or input/output

## ISA Examples


---

- RISC (Reduced Instruction Set Computer)
  - Digital Alpha
  - Sun Sparc
  - MIPS RX000
  - IBM PowerPC
  - HP PA/RISC
- CISC (Complex Instruction Set Computer)
  - Intel x86
  - Motorola 68000
  - DEC VAX
- VLIW (Very Large Instruction Word)
  - Intel Itanium
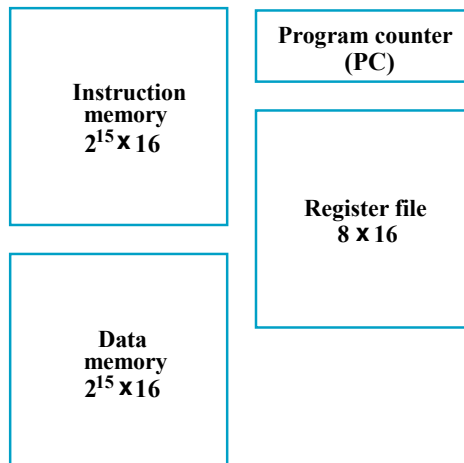
## ISA: Storage Resources


---

- "Harvard architecture": separate instruction and data memories
- Permit use of single clock cycle per instruction implementation
- Due to use of "cache" in modern computer architectures, it is a fairly realistic model



 
## ISA: Instruction Formats


- The three formats are: Register, Immediate, and Jump/Branch



(a) Register

 


(b) Immediate

 

(c) Jump and Branch

- All formats contain an Opcode field in bits 9 through 15.
  - The Opcode specifies the operation to be performed


## ISA: Instruction Format - Register

 

(a) Register

- This format supports:
  - $R1 \leftarrow R2 + R3$
  - $R1 \leftarrow \text{sl } R2$
- Three 3-bit register fields:
  - DR - destination register (R1 in the examples)
  - SA - the A source register (R2 in the first example)
  - SB - the B source register (R3 in the first example and R2 in the second example)
- Why is R2 in the second example SB instead of SA?


## ISA: Instruction Format - Immediate

 

(b) Immediate

- This format supports:
  - $R1 \leftarrow R2 + 3$
- The B Source Register field is replaced by an Operand field OP specifying a constant. (3-bit constant, values from 0 to 7)
- The constant:
  - Zero-fill (on the left of) the operand to form 16-bit constant
  - 16-bit representation for values 0 through 7
 
## ISA: Instruction Format - Jump & Branch



(c) Jump and Branch

- This instruction supports changes in the sequence of instruction execution by adding an extended, 6-bit, signed 2's-complement *address offset* to the PC value
- The SA field: permits jumps and branches on N or Z based on the contents of *Source register A*
- The Address (AD) field (6-bit) replaces the DR and SB fields
  - Example: Suppose that a jump for the Opcode and the PC contains 45 (0...0101101) and AD contains -12 (110100). Then the new PC value will be:  
 $0...0101101 + (1...110100) = 0...0100001$  (i.e.,  $45 + (-12) = 33$ )

## ISA: Instruction Specifications

Instruction	Opcode	Mnemonic	Format	Description	Status Bits
Move A	000000	MOVA	RD,RA	$R[DR] \leftarrow R[SA]$	N, Z
Increment	000001	INC	RD,RA	$R[DR] \leftarrow R[SA] + 1$	N, Z
Add	000010	ADD	RD,RA,SB	$R[DR] \leftarrow R[SA] + R[SB]$	N, Z
Subtract	000011	SUB	RD,RA,SB	$R[DR] \leftarrow R[SA] - R[SB]$	N, Z
Decrement	000110	DEC	RD,RA	$R[DR] \leftarrow R[SA] - 1$	N, Z
AND	000100	AND	RD,RA,SB	$R[DR] \leftarrow R[SA] \wedge R[SB]$	N, Z
OR	000101	OR	RD,RA,SB	$R[DR] \leftarrow R[SA] \vee R[SB]$	N, Z
Exclusive OR	000110	XOR	RD,RA,SB	$R[DR] \leftarrow R[SA] \oplus R[SB]$	N, Z
NOT	000111	NOT	RD,RA	$R[DR] \leftarrow \overline{R[SA]}$	N, Z
Move B	000110	MOVB	RD,RB	$R[DR] \leftarrow R[SB]$	
Shift Right	000111	SHR	RD,RB	$R[DR] \leftarrow sr R[SB]$	
Shift Left	000110	SHL	RD,RB	$R[DR] \leftarrow sl R[SB]$	
Load Immediate	100110	LDI	RD, OP	$R[DR] \leftarrow zf OP$	
Add Immediate	100010	ADI	RD,RA,OP	$R[DR] \leftarrow R[SA] + zf OP$	
Load	001000	LD	RD,RA	$R[DR] \leftarrow M[R[SA]]$	
Store	010000	ST	RA,RB	$M[R[SA]] \leftarrow R[SB]$	
Branch on Zero	110000	BRZ	RA,AD	if $(R[SA] = 0)$ $PC \leftarrow PC + se AD$	
Branch on Negative	110001	BRN	RA,AD	if $(R[SA] < 0)$ $PC \leftarrow PC + se AD$	
Jump	111000	JMP	RA	$PC \leftarrow R[SA]$	

## ISA: Example Instructions and Data in Memory

### Memory Representation of Instruction and Data


Decimal Address	Memory Contents	Decimal Opcode	Other Field	Operation
25	000101 001 010 011	5 (Subtract)	DR:1, SA:2, SB:3	$R1 \leftarrow R2 - R3$
35	010000 000 100 101	32 (Store)	SA:4, SB:5	$M[R4] \leftarrow R5$
45	100010 010 111 011	66 (Add Immediate)	DR: 2, SA :7, OP :3	$R2 \leftarrow R7 + 3$
55	110000 101 110 100	96 (Branch on Zero)	AD: 44, SA:6	If $R6 = 0$ , $PC \leftarrow PC - 20$
70	000000 001100 000	Data = 192. After execution of instruction in 35, Data = 80.		

# Overview

- Part 1 – Datapaths
  - Introduction
  - Datapath Example
    - Arithmetic Logic Unit (ALU)
    - Shifter
  - Datapath Representation and Control Word
  
- Part 2 – A Simple Computer
  - Instruction Set Architecture (ISA)
  - Single-Cycle Hardwired Control
  
- Part 3 – Pipelining
  - Single-Cycle Computer Issues
  - Pipelining concept
  - Pipelined design of Simple Computer
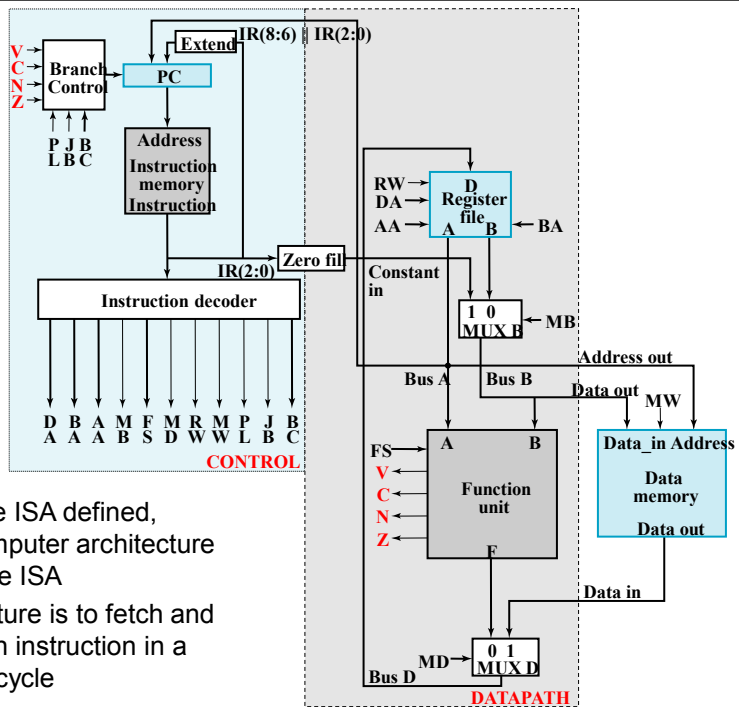
## Single-Cycle Hardwired Control:

- Based on the ISA defined, design a computer architecture to support the ISA
- The architecture is to fetch and execute each instruction in a single clock cycle





## The Control Unit

---

- Datapath: the Data Memory has been attached to the *Address Out*, *Data Out*, and *Data In* lines of the Datapath.
- Control Unit:
  - The *MW* input to the Data Memory is the Memory Write signal from the Control Unit.
  - The Instruction Memory *address* input is provided by the PC and its *instruction output* feeds the Instruction Decoder.
  - Zero-filled IR(2:0) becomes *Constant In*
  - Extended IR(8:6) || IR(2:0) and Bus A are address inputs to the PC.
  - The PC is controlled by Branch Control logic

## Program Counter (PC) Function

---

- PC function is based on instruction specifications involving jumps and branches:
 

<b>Branch on Zero</b>	<b>BRZ</b>	<b>if (R[SA] = 0) PC ← PC + seAD</b>
<b>Branch on Negative</b>	<b>BRN</b>	<b>if (R[SA] &lt; 0) PC ← PC + seAD</b>
<b>Jump</b>	<b>JMP</b>	<b>PC ← R[SA]</b>
- The first two transfers require addition to the PC of:
  - Address Offset = Extended IR(8:6) || IR(2:0)
- The third transfer requires that the PC be loaded with:
  - Jump Address = Bus A = R[SA]
- In addition to the above register transfers, the PC must implement the counting function:
  - PC ← PC + 1

## PC Function (Contd.)

- Branch Control determines the PC transfers based on five inputs:
  - N,Z – negative and zero status bits
  - PL – load enable for the PC
  - JB – Jump/Branch select: If JB = 1, Jump, else Branch
  - BC – Branch Condition select: If BC = 1, branch for N = 1, else branch for Z = 1.

PL	JB	BC	PC Operation
0	X	X	Count Up
1	1	X	Jump
1	0	1	Branch on Negative (else Count Up)
1	0	0	Branch on Zero (else Count Up)

## Instruction Decoder

- Converts the instruction into the signals necessary to control the computer during the single cycle execution, combinational
  - Inputs: the 16-bit Instruction
  - Outputs: control signals
    - DA, AA, and BA: Register file addresses (IR (8:0))
      - simply pass-through signals: DA = DR, AA = SA, and BA = SB
    - FS: Function Unit Select
    - MB and MD: Multiplexer Select Controls
    - RW and MW: Register file and Data Memory Write Controls
    - PL, JB, and BC: PC Controls
- Observe that for other than branches and jumps, FS = IR(12:9)
  - The other control signals should depend as much as possible on IR(15:13)

## Instruction Decoder (Contd.)

Truth Table for Instruction Decoder Logic


Instruction Function Type	Instruction Bits				Control Word Bits							
	15	14	13	9	MB	MD	RW	MW	PL	JB	BC	
1. Function unit operations using registers	0	0	0	X	0	0	1	0	0	X	X	
2. Memory read	0	0	1	X	0	1	1	0	0	X	X	
3. Memory write	0	1	0	X	0	X	0	1	0	X	X	
4. Function unit operations using register and constant	1	0	0	X	1	0	1	0	0	X	X	
5. Conditional branch on zero (Z)	1	1	0	0	X	X	0	0	1	0	0	
6. Conditional branch on negative	1	1	0	1	X	X	0	0	1	0	1	
7. Unconditional Jump <sup>(N)</sup>	1	1	1	X	X	X	0	0	1	1	X	

## Instruction Decoder (Contd.)

- Instruction types are based on the control blocks and the seven control signals to be generated (MB, MD, RW, MW, PL, JB, BC):
  - Datapath and Memory Control (types 1-4)
    - Mux B
    - Memory and Mux D
  - PC Control (types 5-7)
    - Bit 15 = Bit 14 = 1 => PL
    - Bit 13 => JB.
    - Bit 9 was use as BC which contradicts FS = 0000 needed for branches. To force FS(0) to 0 for branches, Bit 9 into FS(0) is disabled by PL.
 
## Instruction Decoder (Contd.)

- The end result by use of the types, careful assignment of codes, and use of don't cares, yields very simple logic:
- This completes the design of most of the essential parts of the single-cycle simple computer





## Example Instruction Execution

### Six Instructions for the Single-Cycle Computer



Operation code	Symbolic Name	Format	Description	Function	MB	MD	RW	MW	PL	JB	BC
1000 010	ADI	Immediate	Add immediate operand	$R[DR] \leftarrow R[SA] + zf / (2:0)$	1	0	1	0	0	0	0
0010 000	LD	Register	Load memory content in to register	$R[DR] \leftarrow M[R[SA]]$	0	1	1	0	0	1	0
0100 000	ST	Register	Store register content in memory	$M[R[SA]] \leftarrow R[SB]$	0	1	0	1	0	0	0
0001 110	SL	Register	Shift left	$R[DR] \leftarrow sl R[SB]$	0	0	1	0	0	1	0
0001 011	NOT	Register	Complement register	$R[DR] \leftarrow \overline{R[SA]}$	0	0	1	0	0	0	1
1100 000	BRZ	Jump/Branch	If $R[SA] = 0$ , branch to PC + se AD	If $R[SA] = 0$ , $PC \leftarrow PC + se AD$ If $R[SA] \neq 0$ , $PC \leftarrow PC + 1$	1	0	0	0	1	0	0

- Decoding, control inputs and paths shown for **ADI**, **LD** and **BRZ** on next 6 slides



# Decoding for ADI

  

# Decoding for LD

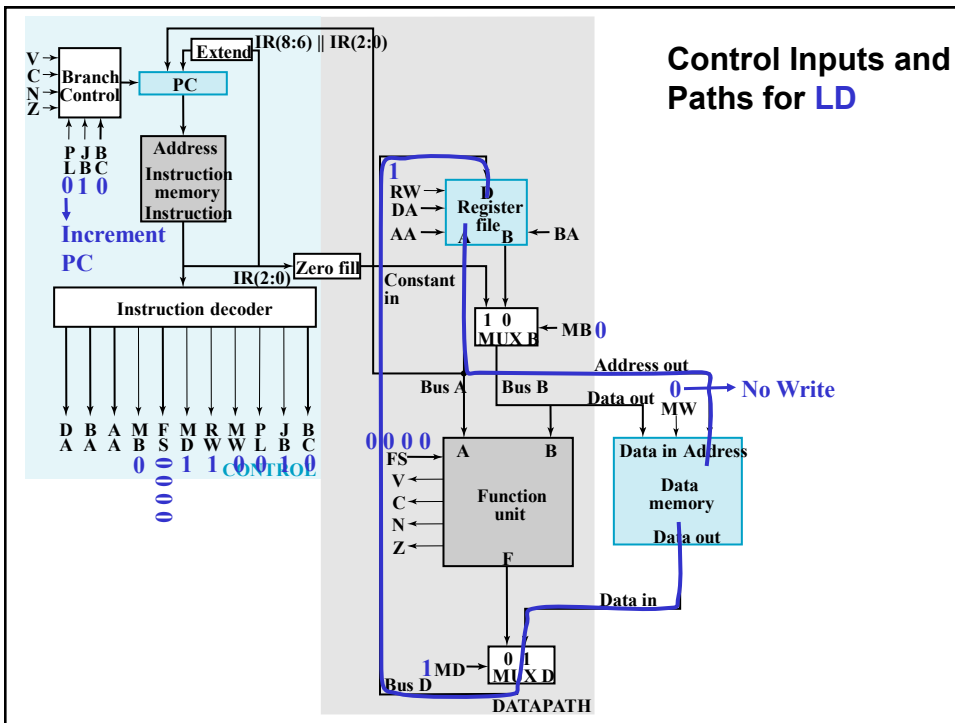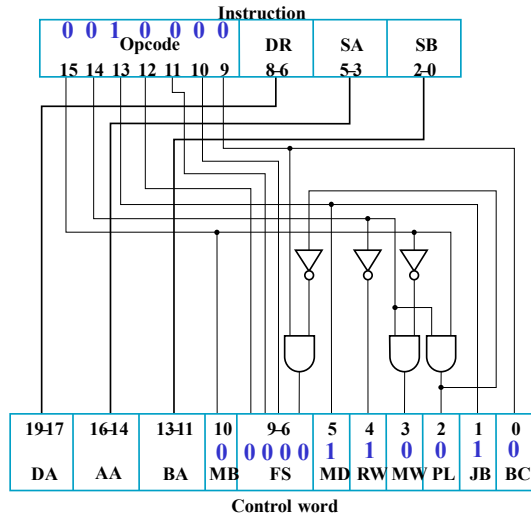

# Decoding for BRZ

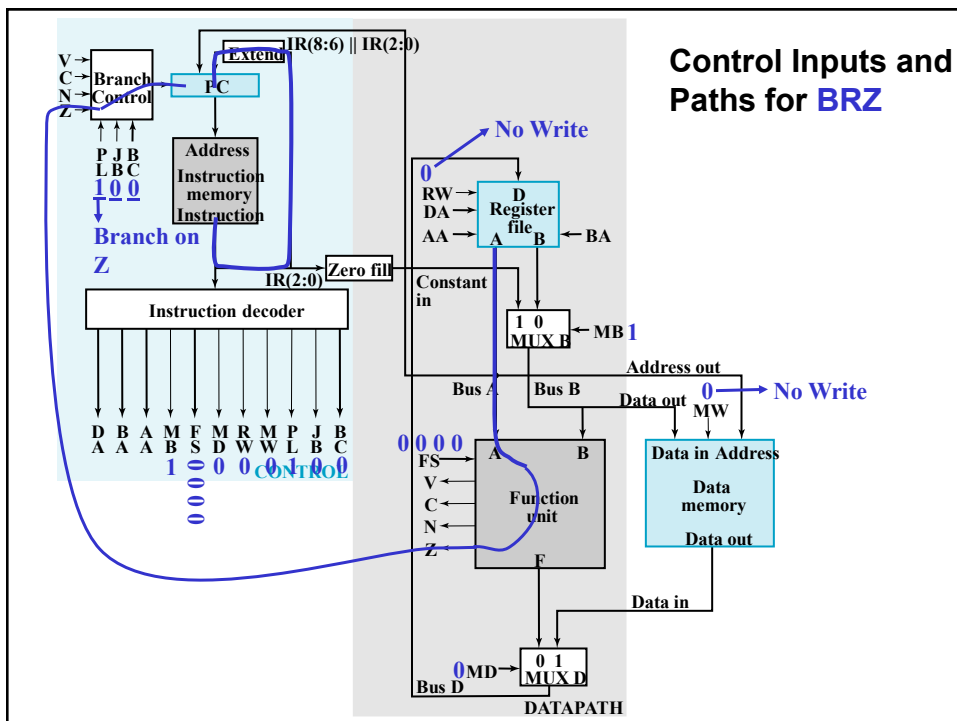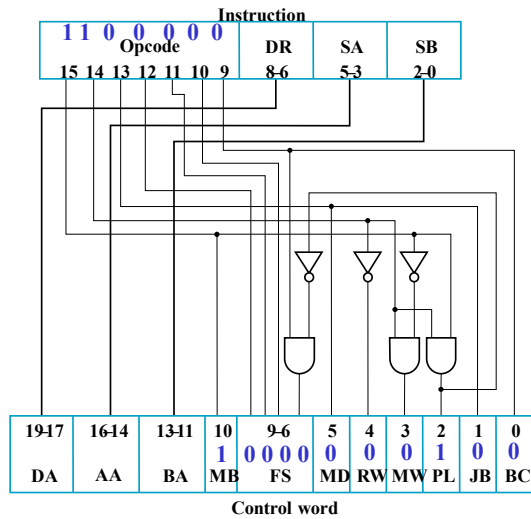

## Overview

---

- Part 1 – Datapaths
  - Introduction
  - Datapath Example
    - Arithmetic Logic Unit (ALU)
    - Shifter
  - Datapath Representation and Control Word
- Part 2 – A Simple Computer
  - Instruction Set Architecture (ISA)
  - Single-Cycle Hardwired Control
- Part 3 – Pipelining
  - Single-Cycle Computer Issues
  - Pipelining concept
  - Pipelined design of Simple Computer

## Single-Cycle Computer Issues

---


- Shortcoming of Single Cycle Design
  - Complexity of instructions executable in a single cycle is limited
  - Accessing both an instruction and data from a simple single memory impossible
  - A long worst case delay path limits clock frequency and the rate of performing instructions
- Handling of Shortcomings
  - The first two shortcomings can be handled by the **multiple-cycle** computer (not covered in these slides)
  - **The third shortcoming is dealt with by using a technique called pipelining**



 
## Pipelining a digital system

---

- Key idea: break big computation into pieces



 
- Separate each piece with a pipeline register


 
## Pipelining a digital system

---

- Why do this? Because it's faster for repeated computations



## Pipelining

---

- Pipelining increases **throughput**, but not total computation time of a task
  - Answer available every 200ps, BUT
  - A single computation still takes 1ns
- Limitations:
  - Computations must be divisible into stage size
  - Pipeline registers add overhead


## Pipelining

---

- **Pipelining transformation** leads to a reduction in the critical path, which can be exploited to increase the clock speed or to reduce power consumption at same speed.
- In parallel processing, multiple outputs are computed in parallel in a clock period. Therefore, the **effective clock speed** is increased by the level of parallelism.

## Example: 3-tap FIR digital filter

 **Example 1:** Consider a 3-tap FIR filter:  $y(n)=ax(n)+bx(n-1)+cx(n-2)$



$T_M$  : multiplication – time

$T_A$  : Addition – time

- The critical path (or the minimum time required for processing a new sample) is limited by 1 multiply and 2 add times. Thus, the “sample period” (or the “sample frequency”) is given by:


$$T_{sample} \geq T_M + 2 T_A$$

$$f_{sample} \leq \frac{1}{T_M + 2 T_A}$$

## Example: 3-tap FIR digital filter

- The pipelined implementation: By introducing 2 additional latches in Example 1, the critical path is reduced from  $T_M+2T_A$  to  $T_M+T_A$ . The schedule of events for this pipelined system is shown in the following table. You can see that, at any time, 2 consecutive outputs are computed in an interleaved manner.

Clock	Input	Node 1	Node 2	Node 3	Output
0	$x(0)$	$ax(0)+bx(-1)$	—	—	—
1	$x(1)$	$ax(1)+bx(0)$	$ax(0)+bx(-1)$	$cx(-2)$	$y(0)$
2	$x(2)$	$ax(2)+bx(1)$	$ax(1)+bx(0)$	$cx(-1)$	$y(1)$
3	$x(3)$	$ax(3)+bx(2)$	$ax(2)+bx(1)$	$cx(0)$	$y(2)$

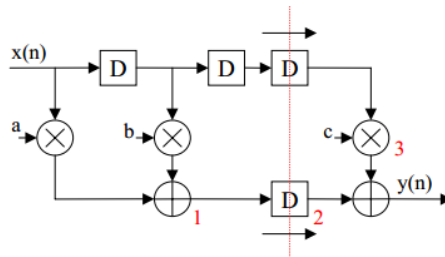


## The Laundry Analogy

- Ann, Brian, Cathy, Dave each have one load of clothes to wash, dry, and fold
- Washer takes 30 minutes
- Dryer takes 30 minutes
- “Folder” takes 30 minutes
- “Stasher” takes 30 minutes to put clothes into drawers




## If we do laundry sequentially...

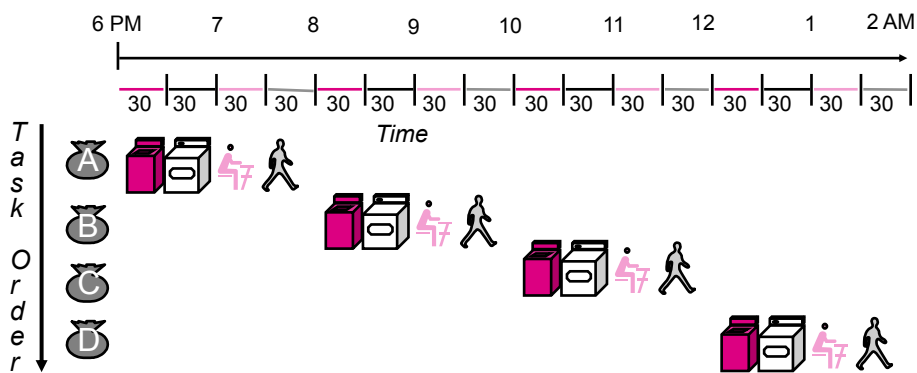


- Time Required: 8 hours for 4 loads

## To Pipeline, We Overlap Tasks

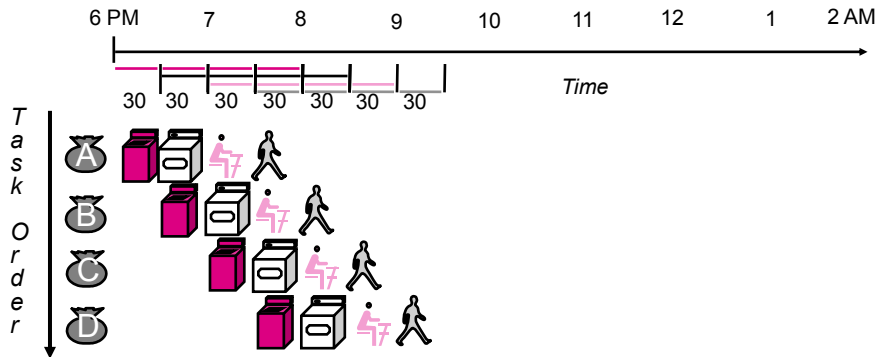

- Time Required: 3.5 Hours for 4 Loads

## To Pipeline, We Overlap Tasks

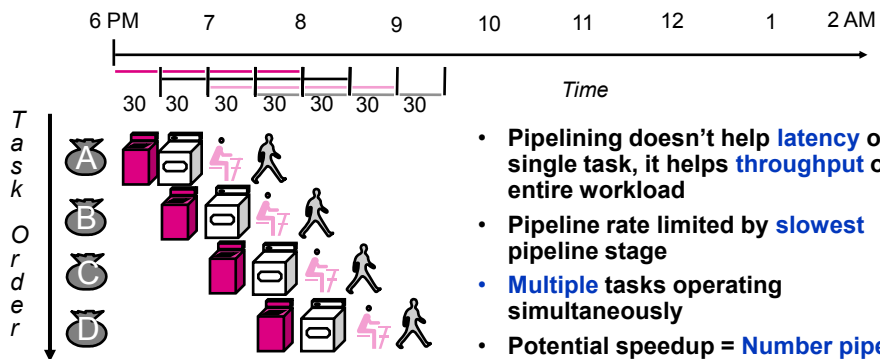


- Pipelining doesn't help **latency** of single task, it helps **throughput** of entire workload
- Pipeline rate limited by **slowest** pipeline stage
- **Multiple** tasks operating simultaneously
- Potential speedup = **Number pipe stages**
- Unbalanced lengths of pipe stages reduces speedup
- Time to "**fill**" pipeline and time to "**drain**" it reduces speedup

## Overview

- Part 1 – Datapaths
  - Introduction
  - Datapath Example
    - Arithmetic Logic Unit (ALU)
    - Shifter
  - Datapath Representation and Control Word
  
- Part 2 – A Simple Computer
  - Instruction Set Architecture (ISA)
  - Single-Cycle Hardwired Control
  
- Part 3 – Pipelining
  - Single-Cycle Computer Issues
  - Pipelining concept
  - **Pipelined design of Simple Computer**
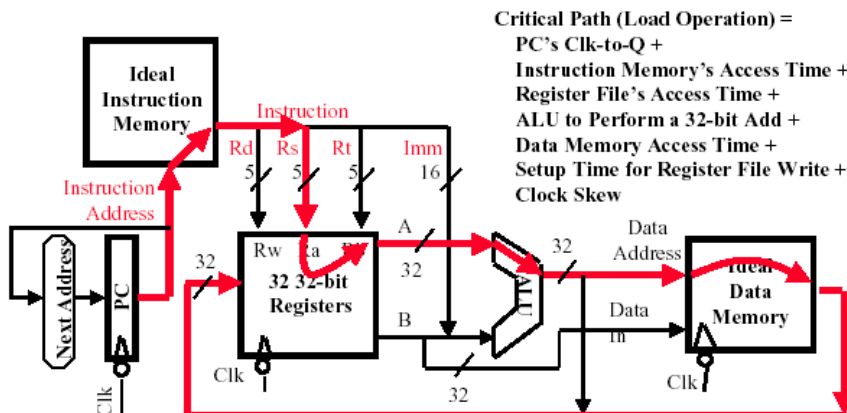
## Abstract View of Critical Path

- Register file and ideal memory:
  - The CLK input is a factor ONLY during write operation
  - During read operation, behave as combinational logic:
    - Address valid => Output valid after “access time.”





## Un-pipelined (Non-overlapped) Implementation

---

- Consider loads with DF stage

	C1	C2	C3	C4	C5	C6	C7	C8	C9	C10
I1	IF	DR	E	DF	W					
I2						IF	DR	E	DF	W
I3										
...										

## Pipelined Implementation

---


	C1	C2	C3	C4	C5	C6	C7	C8	C9	C10
I1	IF	DR	E	DF	W					
I2		IF	DR	E	DF	W				
I3			IF	DR	E	DF	W			
I4				IF	DR	E	DF	W		
I5					IF	DR	E	DF	W	
I6						IF	DR	E	DF	W


 
## 5-stage Pipeline

---

- CPU stages
  - IF: Instruction fetch
  - DR: Instruction decode & Register read
  - E: Execute
  - DF: Data fetch (Memory load/store)
  - W: Write Back Registers
- Another set of mnemonic names
  - IF, ID, E, MEM, WB



## Computer Pipelines

---

- Execute billions of instructions, so **throughput** is what matters
- Throughput versus latency
  - + Throughput increases
  - - Latency for a single instruction increases
    - May have to wait longer for single instruction to complete
- Allows much faster clock cycle
- RISC pipeline architecture features:
  - All instructions same length
  - Registers located in same place in instruction format
  - Memory operands only in loads and stores

## Summary

---

- Concept of Datapath for implementing computer microinstructions
- Control word provides a means of organizing the control of the microoperations
- Concept of ISA and instruction formats and operations of Simple Computer (SC)
- Pipelining

## For Adventurers

---

- I have a VHDL implementation of the Single Cycle Computer (SCC) described in this presentation. It's verified via simulation and actual hardware implementation on an FPGA (Spartan-6)
- If you are interested in studying it via simulation:
  - Download and install the free Aldec-HDL simulator as described here:
    - [http://dejazzter.com/ee478/labs/lab1\\_aldec\\_tutorial.pdf](http://dejazzter.com/ee478/labs/lab1_aldec_tutorial.pdf)
  - Then, simulate the SCC using the VHDL source code available for download here:
    - [http://dejazzter.com/ee478/labs/lab11\\_files.zip](http://dejazzter.com/ee478/labs/lab11_files.zip)