

# EE 459/500 – HDL Based Digital Design with Programmable Logic

---

## Lecture 10 Arithmetic Units

*Read before class:*

*First part of Chapter 4 from textbook*

### Overview

---

- Adders/Subtractors
- Multipliers
- Xilinx Unisim

## Adders/Subtractors - Integers

---

- Basic building block for Computer-Arithmetic and Digital Signal Processing
- Operate on binary vectors; use the same sub-function in each bit position


## Adder Design

---

- Functional blocks:
  - Half-Adder (HA): a 2-input bitwise addition
  - Full-Adder (FA): a 3-input bit-wise addition
- **Ripple-carry adder**: an iterative array to perform binary addition, full adders chained together
- **Carry-look-ahead adder**: a hierarchical adder to improve performance
  - Propagate and generate logic

## Functional Block Implementation

- Half adder:

 



- Full adder:

$$S = X \oplus Y \oplus C_{in}$$

$$C = XY + (X \oplus Y)C_{in}$$


$$= G + P \cdot C_{in}$$

  - $XY$ : carry generate  $G$
- $X \oplus Y$ : carry propagate  $P$



 
## Ripple Carry Adder

- A 4-bit ripple carry adder made from four 1-bit full adder



 - Worst case delay: #bits x (full adder delay)
  - The longest path is from  $A_0/B_0$  through the circuit to  $S_3$
  - Or from  $C_0$  through the circuit to  $C_4$ .



## Carry Lookahead Adder

- From the full-adder implementation, two signal conditions: *generate*  $G$  and *propagate*  $P$ .

$$\begin{array}{l} P_i = A_i \oplus B_i \\ G_i = A_i B_i \end{array} \quad \longrightarrow \quad \begin{array}{l} S_i = P_i \oplus C_i \\ C_{i+1} = G_i + P_i C_i \end{array}$$

- In order to reduce the length of the carry chain,  $C_i$  is changed to a more global function spanning multiple cells

$$C_1 = G_0 + P_0 C_0$$

$$C_2 = G_1 + P_1 C_1 = G_1 + P_1 (G_0 + P_0 C_0)$$


$$= G_1 + P_1 G_0 + P_1 P_0 C_0 = G_{0-2} + P_{0-2} C_0$$

$$C_3 = G_2 + P_2 C_2 = G_2 + P_2 (G_1 + P_1 G_0 + P_1 P_0 C_0)$$

$$= G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0 = G_{0-3} + P_{0-3} C_0$$

$$C_4 = G_3 + P_3 C_3 = G_3 + P_3 (G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0)$$
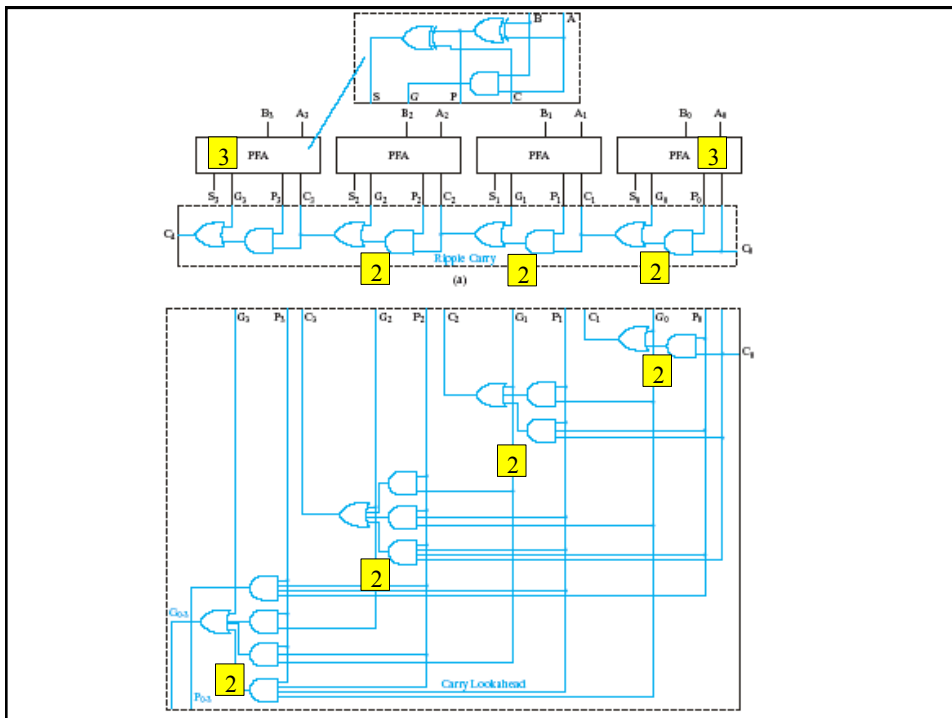
$$= G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 C_0 = G_{0-4} + P_{0-4} C_0$$



## VHDL Description of a 4-bit CLA

```
entity CLA4 is
  port (A, B: in bit_vector (3 downto 0); Ci: in bit;
        S: out bit_vector (3 downto 0); Co, PG, GG: out bit);
end CLA4;

architecture structure of CLA4 is
  component GPFullAdder
    port (X, Y, Cin: in bit;
          G, P, Sum: out bit);
  end component;
  component CLALogic is
    port (G, P: in bit_vector (3 downto 0); Ci: in bit;
          C: out bit_vector (3 downto 1); Co, FG, CG: out bit);
  end component;
  signal G, P: bit_vector (3 downto 0);
  signal C: bit_vector (3 downto 0);
begin
  CarryLogic: CLALogic port map (G, P, Ci, C, Co, PG, GG);
  FA0: GPFullAdder port map (A(0), B(0), Ci, G(0), P(0), S(0));
  FA1: GPFullAdder port map (A(1), B(1), C(1), G(1), P(1), S(1));
  FA2: GPFullAdder port map (A(2), B(2), C(2), G(2), P(2), S(2));
  FA3: GPFullAdder port map (A(3), B(3), C(3), G(3), P(3), S(3));
end structure;
```


## CLALogic

```
entity CLALogic is
  port (G, P: in bit_vector (3 downto 0); Ci: in bit;
        C: out bit_vector (3 downto 1); Co, PG, GG: out bit);
end CLALogic;

architecture Equations of CLALogic is
  signal GG_int, PG_int: bit
begin
  C(1) <= G(0) or (P(0) and Ci);
  C(2) <= G(1) or (P(1) and G(0) or (P(1) and P(0) and Ci));
  C(3) <= G(2) or (P(2) and P(1) and G(0) or (P(2) and P(1) and P(0)
  and Ci));
  PG_int <= P(3) and P(2) and P(1) and P(0);
  GG_int <= G(3) or (P(3) and G(2)) or (P(3) and P(2) and G(1)) or
  (P(3) and P(2) and P(1) and P(0) and G(0));
  Co <= GG_int or (PG_int and Ci);
  PG <= PG_int;
  GG <= GG_int;
end Equations;
```
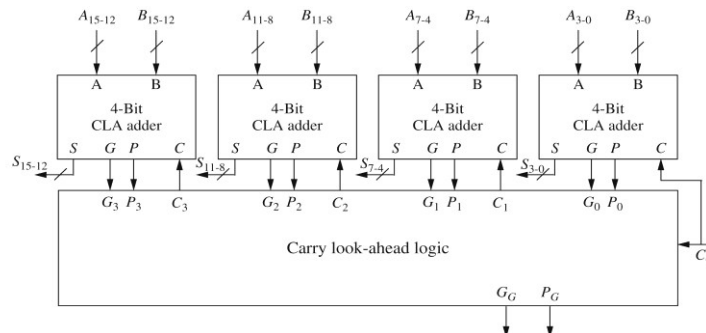
## 16-bit Carry Lookahead Adder

- Extend to 16 bits, to have four 4-bit adders use one of the same carry lookahead circuits
- Delay Specifications
  - NOT=1, XOR=3 AND=3, AND-OR=2
- Longest delays:
  - Ripple carry adder =  $3+15*2+3=36$
  - CLA =  $3+3*2+3=12$



## Subtraction

- Subtraction (A-B)
  - Unsigned:
    - $A \geq B \Rightarrow A-B$
    - $A < B \Rightarrow$  the difference  $A-B+2^n$  is subtracted from  $2^n$ , a “-” sign added before the result ( $2^n-X$  is taking the 2’s complement of X)
  - Signed integer
    - For binary numbers
      - $s a_{n-2} \dots a_2 a_1 a_0$
      - $s=0$  for positive numbers;
      - $s=1$  for negative numbers
    - Signed-magnitude: the n-1 digits are a positive magnitude
    - Signed 2’s complement



## VHDL code for adder/subtractor

```
-- add/subtract select to carry input (S = 1 for subtract)
C(0) <= S;

adders:
FOR i IN 1 to 4 GENERATE
  --invert B for subtract function (B(i) xor 1,)
  --do not invert B for add function (B(i) xor 0)
  B_comp(i) <= B(i) xor S;
  adder: full_add PORT MAP (A(i),B_comp(i),C(I -1),C(i),Sout(i));
END GENERATE;

Cout <= C(4);

END structural;
```

## VHDL code for adder/subtractor

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY addsubtract IS
PORT ( S      : IN  STD_LOGIC;
      A, B    : IN  STD_LOGIC_VECTOR (3 DOWNTO 0);
      Sout    : OUT STD_LOGIC_VECTOR (3 DOWNTO 0);
      Cout   : OUT STD_LOGIC);
END adderlpm;

ARCHITECTURE behavioral OF addsubtract IS
signal Sum : STD_LOGIC_VECTOR (4 downto 0);
BEGIN
with S select
  Sum <= A + B when '0'
        A - B + "10000" when others;
Cout <= Sum(4);
Sout <= Sum(3 downto 0);
END behavioral;
```



## Overview

---

- Adders/Subtractors
- **Multipliers**
- Xilinx Unisim

## Multiplication


---

- Multiply requires shifting the multiplicand to the left adding it to the partial sum
- Requires a shift register as wide as the product and an accumulator for the partial and final product.


$$\begin{array}{r} \text{Multiplicand} \longrightarrow 1\ 1\ 0\ 1\ (13) \\ \text{Multiplier} \longrightarrow 1\ 0\ 1\ 1\ (11) \\ \hline \text{Partial products } \left. \begin{array}{l} \longrightarrow 1\ 1\ 0\ 1 \\ \longrightarrow 1\ 1\ 0\ 1 \\ \longrightarrow 1\ 0\ 0\ 1\ 1\ 1 \\ \longrightarrow 0\ 0\ 0\ 0 \\ \longrightarrow 1\ 0\ 0\ 1\ 1\ 1 \\ \longrightarrow 1\ 1\ 0\ 1 \end{array} \right\} \\ \hline 1\ 0\ 0\ 0\ 1\ 1\ 1\ 1\ (143) \end{array}$$
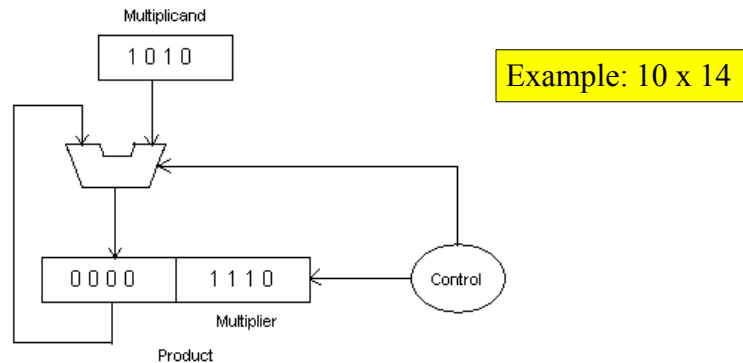
## Add-and-Shift Multiplier


- Place the multiplier in the rightmost 4 bits of the 8-bit product register



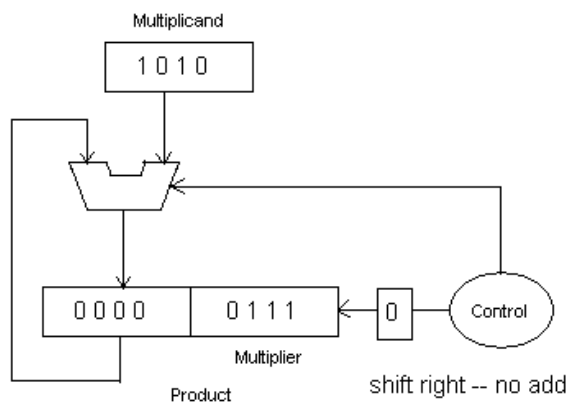
- Shift 1 -- The bit shifted out of the product register is 0. No add is performed.



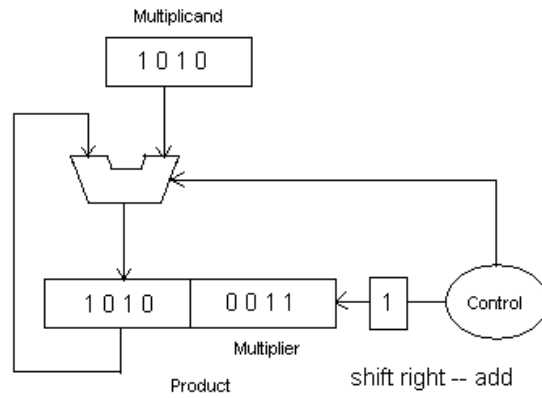
- Shift 2 -- The bit shifted out of the product register is 1. Add the multiplicand to the first 4 bits of the product register.



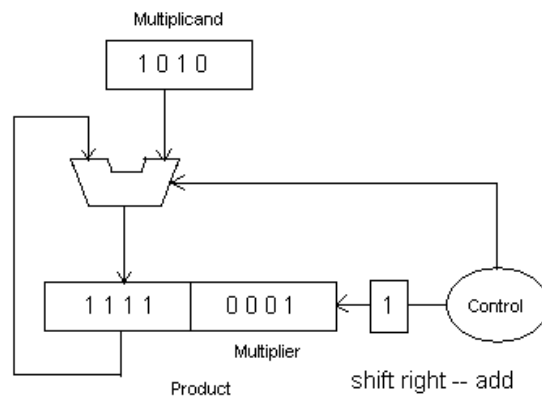
- Shift 3 -- Again add the multiplicand to the leftmost 4 bits of the product register.



- Shift 4 -- Shift then add.

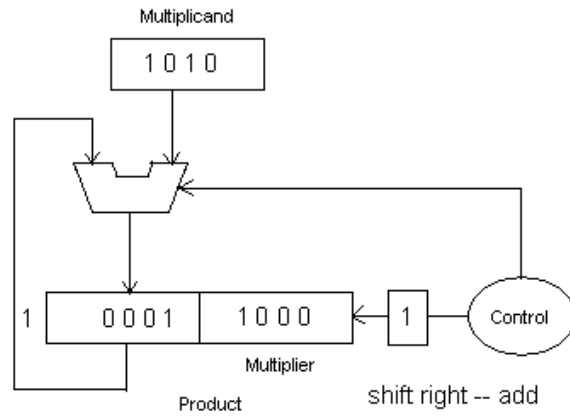


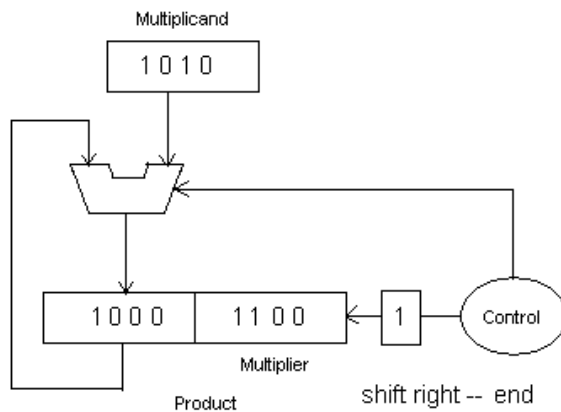- Finally, shift right and end. The product is found in the 8-bit product register (140)



$$10 \times 14 = 140$$

## Add-and-Shift Multiplier

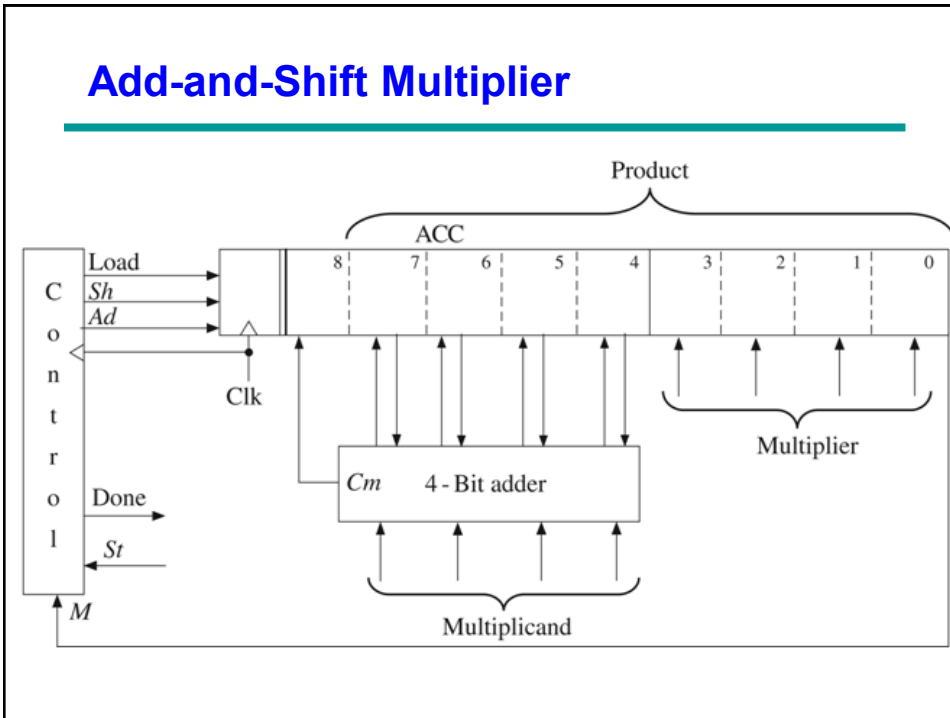

## Add-and-Shift Multiplier

initial contents of product register	0 0 0 0 0   1 0 1 1	← M (11)
(add multiplicand since M = 1)	1 1 0 1	(13)
after addition	0 1 1 0 1   1 0 1 1	
after shift	0 0 1 1 0 1   1 0 1	← M
(add multiplicand since M = 1)	1 1 0 1	
after addition	1 0 0 1 1 1   1 0 1	
after shift	0 1 0 0 1 1 1   1 0	← M
(skip addition since M = 0)		
after shift	0 0 1 0 0 1 1 1   1	← M
(add multiplicand since M = 1)	1 1 0 1	
after addition	1 0 0 0 1 1 1 1   1	
after shift (final answer)	0 1 0 0 0 1 1 1 1	(143)

dividing line between product and multiplier

## State Graph

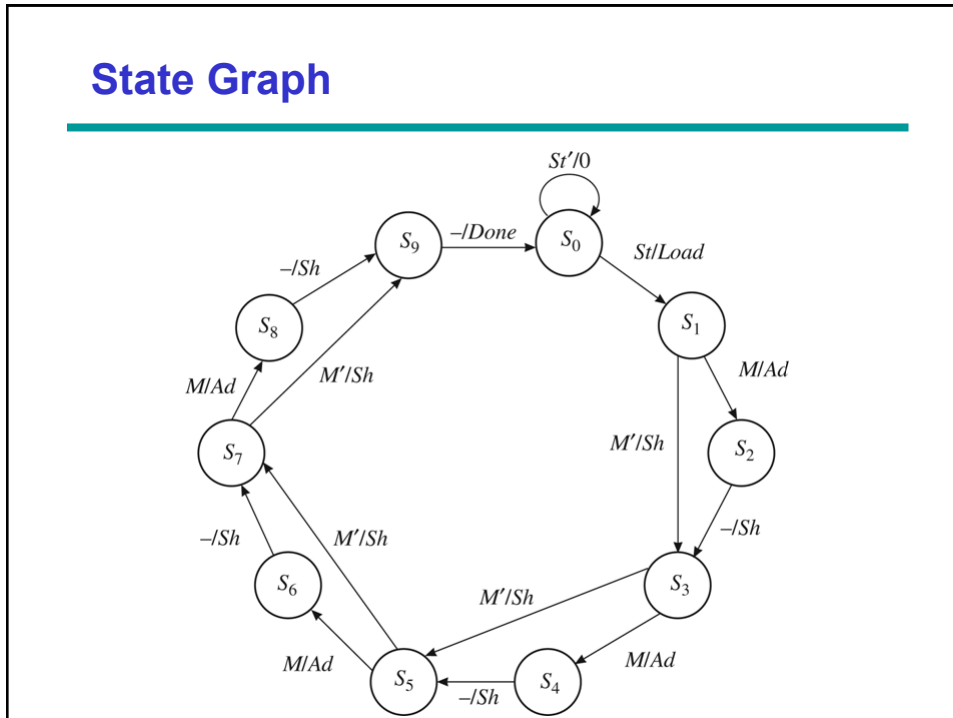


FIGURE 4-27: Behavioral Model for  $4 \times 4$  Binary Multiplier

```
-- This is a behavioral model of a multiplier for unsigned
-- binary numbers. It multiplies a 4-bit multiplicand
-- by a 4-bit multiplier to give an 8-bit product.
```

```
-- The maximum number of clock cycles needed for a
-- multiply is 10.
```

```
library IEEE;
use IEEE.numeric_bit.all;
```

```
entity mult4X4 is
  port(Clk, St: in bit;
        Mplier, Mcand: in unsigned(3 downto 0);
        Done: out bit);
end mult4X4;
```

```
architecture behavel of mult4X4 is
  signal State: integer range 0 to 9;
  signal ACC: unsigned(8 downto 0); -- accumulator
  alias M: bit is ACC(0); -- M is bit 0 of ACC
```

```
begin
  process(Clk)
  begin
    if Clk'event and Clk = '1' then -- executes on rising edge of clock
      case State is
        when 0 => -- initial State
          if St = '1' then
            ACC(8 downto 4) <= "00000"; -- begin cycle
            ACC(3 downto 0) <= Mplier; -- load the multiplier
            State <= 1;
          end if;
        end if;
```

## VHDL code for 4-bit binary multiplier

```


when 1 | 3 | 5 | 7 => -- "add/shift" State
  if M = '1' then -- add multiplicand
    ACC(8 downto 4) <= '0' & ACC(7 downto 4) + Mcand;
    State <= State + 1;
  else
    ACC <= '0' & ACC(8 downto 1); -- shift accumulator right
    State <= State + 2;
  end if;
when 2 | 4 | 6 | 8 => -- "shift" State
  ACC <= '0' & ACC(8 downto 1); -- right shift
  State <= State + 1;
when 9 => -- end of cycle
  State <= 0;
end case;
end process;
Done <= '1' when State = 9 else '0';
end behave1;

```

## Array Multiplier

			$X_3$	$X_2$	$X_1$	$X_0$		
			$Y_3$	$Y_2$	$Y_1$	$Y_0$	Multiplicand	
			$X_3Y_0$	$X_2Y_0$	$X_1Y_0$	$X_0Y_0$	Multiplier	
	$X_3Y_1$		$X_2Y_1$	$X_1Y_1$	$X_0Y_1$		Partial product 0	
	$C_{12}$		$C_{11}$	$C_{10}$			Partial product 1	
	$C_{13}$	$S_{13}$	$S_{12}$	$S_{11}$	$S_{10}$		First row carries	
	$X_3Y_2$		$X_2Y_2$	$X_1Y_2$	$X_0Y_2$		First row sums	
	$C_{22}$		$C_{21}$	$C_{20}$			Partial product 2	
	$C_{23}$	$S_{23}$	$S_{22}$	$S_{21}$	$S_{20}$		Second row carries	
	$X_3Y_3$		$X_2Y_3$	$X_1Y_3$	$X_0Y_3$		Second row sums	
	$C_{32}$		$C_{31}$	$C_{30}$			Partial product 3	
	$C_{33}$	$S_{33}$	$S_{32}$	$S_{31}$	$S_{30}$		Third row carries	
	$P_7$	$P_6$	$P_5$	$P_4$	$P_3$	$P_2$	$P_1$	$P_0$
								Third row sums
								Final product

## Array Multiplier

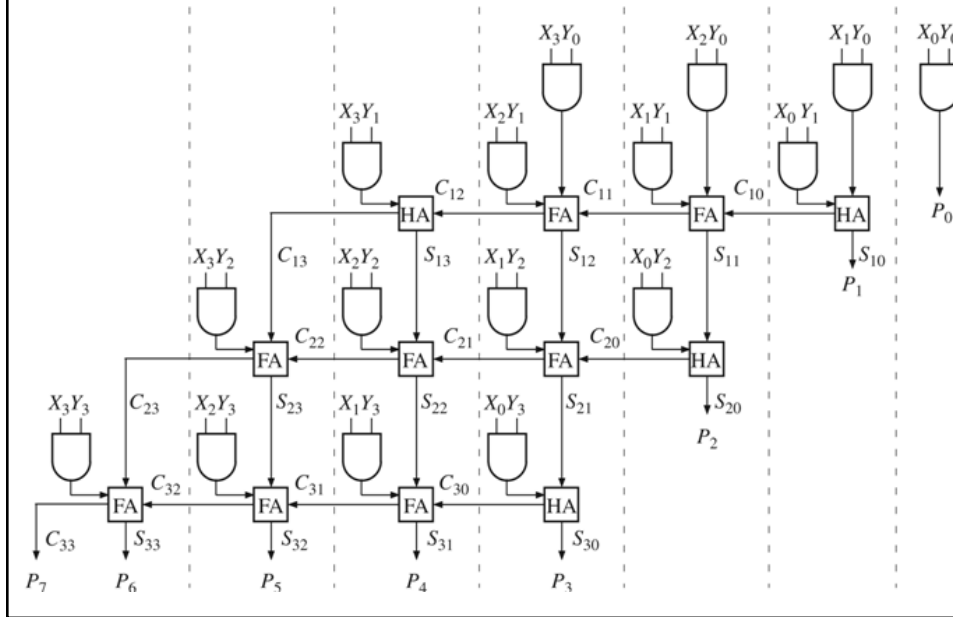

```

entity Array_Mult is
    port(X, Y: in bit_vector(3 downto 0);
          P: out bit_vector(7 downto 0));
end Array_Mult;

architecture Behavioral of Array_Mult is
    signal C1, C2, C3: bit_vector(3 downto 0);
    signal S1, S2, S3: bit_vector(3 downto 0);
    signal XY0, XY1, XY2, XY3: bit_vector(3 downto 0);
    component FullAdder
        port(X, Y, Cin: in bit;
              Cout, Sum: out bit);
    end component;
    component HalfAdder
        port(X, Y: in bit;
              Cout, Sum: out bit);
    end component;
begin
    XY0(0) <= X(0) and Y(0); XY1(0) <= X(0) and Y(1);
    XY0(1) <= X(1) and Y(0); XY1(1) <= X(1) and Y(1);
    XY0(2) <= X(2) and Y(0); XY1(2) <= X(2) and Y(1);
    XY0(3) <= X(3) and Y(0); XY1(3) <= X(3) and Y(1);

    XY2(0) <= X(0) and Y(2); XY3(0) <= X(0) and Y(3);
    XY2(1) <= X(1) and Y(2); XY3(1) <= X(1) and Y(3);
    XY2(2) <= X(2) and Y(2); XY3(2) <= X(2) and Y(3);
    XY2(3) <= X(3) and Y(2); XY3(3) <= X(3) and Y(3);

    FA1: FullAdder port map (XY0(2), XY1(1), C1(0), C1(1), S1(1));
    FA2: FullAdder port map (XY0(3), XY1(2), C1(1), C1(2), S1(2));
    FA3: FullAdder port map (S1(2), XY2(1), C2(0), C2(1), S2(1));
    FA4: FullAdder port map (S1(3), XY2(2), C2(1), C2(2), S2(2));
    FA5: FullAdder port map (C1(3), XY2(3), C2(2), C2(3), S2(3));
    FA6: FullAdder port map (S2(2), XY3(1), C3(0), C3(1), S3(1));
    FA7: FullAdder port map (S2(3), XY3(2), C3(1), C3(2), S3(2));
    FA8: FullAdder port map (C2(3), XY3(3), C3(2), C3(3), S3(3));
    HA1: HalfAdder port map (XY0(1), XY1(0), C1(0), S1(0));
    HA2: HalfAdder port map (XY1(3), C1(2), C1(3), S1(3));
    HA3: HalfAdder port map (S1(1), XY2(0), C2(0), S2(0));
    HA4: HalfAdder port map (S2(1), XY3(0), C3(0), S3(0));

    P(0) <= XY0(0); P(1) <= S1(0); P(2) <= S2(0);
    P(3) <= S3(0); P(4) <= S3(1); P(5) <= S3(2);
    P(6) <= S3(3); P(7) <= C3(3);
end Behavioral;

-- Full Adder and half adder entity and architecture descriptions
-- should be in the project
    
```

## VHDL code for 4-bit array multiplier



## VHDL code for 4-bit array multiplier

```
entity FullAdder is
  port(X, Y, Cin: in bit;
        Cout, Sum: out bit);
end FullAdder;

architecture equations of FullAdder is
begin
  Sum <= X xor Y xor Cin;
  Cout <= (X and Y) or (X and Cin) or (Y and Cin);
end equations;

entity HalfAdder is
  port(X, Y: in bit;
        Cout, Sum: out bit);
end HalfAdder;

architecture equations of HalfAdder is
begin
  Sum <= X xor Y;
  Cout <= X and Y;
end equations;
```

## Overview

---

- Adders/Subtractors
- Multipliers
- Xilinx Unisim

## Xilinx simulation libraries

---

- Xilinx provides the following simulation libraries for simulating primitives and cores ([http://www.xilinx.com/support/documentation/sw\\_manuals/xilinx11/ise\\_c\\_simulation\\_libraries.htm](http://www.xilinx.com/support/documentation/sw_manuals/xilinx11/ise_c_simulation_libraries.htm)):
  - **UNISIM library** for functional simulation of Xilinx primitives
  - UniMacro library for functional simulation of Xilinx macros
  - XilinxCoreLib library for functional simulation of Xilinx cores
  - Xilinx EDK library for behavioral simulation of Xilinx Embedded Development Kit (EDK) IP components
  - SIMPRIM library for timing simulation of Xilinx primitives
  - SmartModel/SecureIP simulation library for both functional and timing simulation of Xilinx Hard-IP, such as PPC, PCIe, GT, and TEMAC IP.

## Xilinx Unisim Library of Primitives

---

- Xilinx ISE XST system includes a library of primitives and macros called **Unisim**
- Many modules in the library are technology dependent
- Most modules are **parameterized**
- More modules are available through CoreGenerator (see also Lab #5 of this course)
- Spartan-6 Libraries Guide for HDL Designs: [http://www.xilinx.com/support/documentation/sw\\_manuals/xilinx11/spartan6\\_hdl.pdf](http://www.xilinx.com/support/documentation/sw_manuals/xilinx11/spartan6_hdl.pdf)

## Example: VHDL Instantiation Template

```
library UNIMACRO;
use unimacro.vcomponents.all;

-- ADDMACC_MACRO: Add and Multiple Accumulate Function implemented in a DSP48E
--                Virtex-6, Spartan-6
-- Xilinx HDL Libraries Guide, version 11.2

ADDMACC_MACRO_inst : ADDMACC_MACRO
generic map (
  DEVICE => "VIRTEX6", -- Target Device: "VIRTEX6", "SPARTAN6"
  LATENCY => 3, -- Desired clock cycle latency, 1-4
  WIDTH_PREADD => 18, -- Pre-Adder input bus width, 1-25
  WIDTH_MULTIPLIER => 18, -- Multiplier input bus width, 1-18
  WIDTH_PRODUCT => 48) -- Product output bus width, 1-48
port map (
  PRODUCT => PRODUCT, -- ADDMACC ouput bus, width determined by WIDTH_PRODUCT generic
  MULTIPLIER => MULTIPLIER, -- MULTIPLIER input bus, width determined by WIDTH_MULTIPLIER generic
  PREADDER1 => PREADDER1, -- 1st Pre-Adder input bus, width determined by WIDTH_PREADDER generic
  PREADDER2 => PREADDER2, -- 2nd Pre-Adder input bus, width determined by WIDTH_PREADDER generic
  CARRYIN => CARRYIN, -- 1-bit carry-in input to accumulator
  CE => CE, -- 1-bit active high input clock enable
  CLK => CLK, -- 1-bit positive edge clock input
  LOAD => LOAD, -- 1-bit active high input load accumulator enable
  LOAD_DATA => LOAD_DATA, -- Load accumulator input data,
  RST => RST -- 1-bit input active high reset
);
-- End of ADDMACC_MACRO_inst instantiation
```

Always check documentation for your FPGA family to see what's available!

## Example: Spartan-3E FPGA

- Use primitive named "RAMB16\_S2" (an 8k x 2 Single-Port RAM for Spartan-3E FPGA) to create an 8k x 4 single port RAM

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;
use ieee.std_logic_arith.all;

library unisim;
use unisim.vcomponents.all;

entity ram_test is
end ram_test;
```

```

architecture Behavioral of ram_test is

--signal declarations.
signal clk, en, ssr, we : std_logic:= '0';
signal Dout, Din : std_logic_vector(3 downto 0):="0000";
signal addr : std_logic_vector(12 downto 0):=(others => '0');

begin

--RAMB16_S2 is 8k x 2 Single-for Spartan-3E.
--We use this to create 8k x 4 Single-Port RAMPort RAM.
--Initialize RAM which carries LSB 2 bits of the data.
RAM1 : RAMB16_S2 port map (
    DO => Dout(1 downto 0),      -- 2-bit Data Output
    ADDR => ADDR,                -- 13-bit Address Input
    CLK => CLK,                  -- Clock
    DI => Din(1 downto 0),      -- 2-bit Data Input
    EN => EN,                    -- RAM Enable Input
    SSR => SSR,                  -- Synchronous Set/Reset Input
    WE => WE                      -- Write Enable Input
)

--Initialize RAM which carries MSB 2 bits of the data.
RAM2 : RAMB16_S2 port map (
    DO => Dout(3 downto 2),      -- 2-bit Data Output
    ADDR => ADDR,                -- 13-bit Address Input
    CLK => CLK,
    DI => Din(3 downto 2),
    EN => EN,
    SSR => SSR,
    WE => WE
);

```

```

--100 MHz clock generation for testing process.
clk_process : process
begin
    wait for 5 ns;
    clk <= not clk;
end process;

--Write and Read.
--RAM has a depth of 13 bits and has a width of 4 bits.
simulate : process
begin
    en <= '1';
    we <= '1';
    --Write the value "i" at the address "i" for 10 clock cycles.
    for i in 0 to 10 loop
        addr <= conv_std_logic_vector(i,13);
        din <= conv_std_logic_vector(i,4);
        wait for 10 ns;
    end loop;
    we <= '0';
    --Read the RAM for addresses from 0 to 20.
    for i in 0 to 20 loop
        addr <= conv_std_logic_vector(i,13);
        wait for 10 ns;
    end loop;

end process;

end Behavioral;

```

## Summary

---

- Adders/subtractors are very important arithmetic units utilized in a variety of applications (processors, DSPs, etc.)
- More ways to design them; tradeoffs between area and performance
- Always check documentation for your FPGA family

## Appendix A: Other Arithmetic Functions

---

- **Overflow detection:** overflow occurs if  $n+1$  bits are required to contain the results from an  $n$ -bit addition or subtraction
- **Incrementing:** counting up,  $A+1$ ,  $B+4$
- **Decrementing:** counting down,  $A-1$ ,  $B-4$
- **Multiplication by constant:** left shift
- **Division by constant:** right shift
- **Zero fill:** filling zero either at MSB or LSB end
- **Extension:** copy the MSB of the operand into the new positions