

EE 459/500 – HDL Based Digital Design with Programmable Logic

Lecture 13

Control and Sequencing: Hardwired and Microprogrammed Control

References:


Chapter s 4,5 from textbook

Chapter 7 of M.M. Mano and C.R. Kime, Logic and Computer Design Fundamentals, Pearson Prentice-Hall, 2008.

Overview

- Control and Sequencing
 - Algorithmic State Machine (ASM) Chart of Multiplier
 - Hardwired control
 - Microprogrammed control


Multiplier Example: Block Diagram

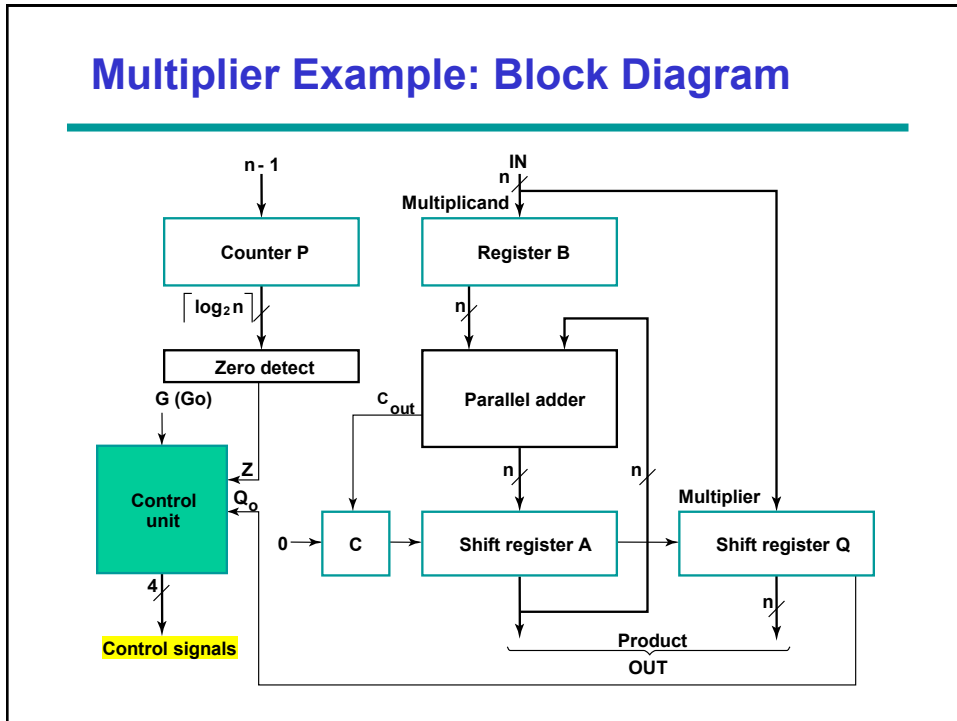

Multiplier Example: Operation

1. The multiplicand is loaded into register B.
2. The multiplier is loaded into register Q.
3. When G becomes 1, register C||A is initialized to 0.
4. Down Counter P is initialized to $n - 1$ (n = number of bits in multiplier)
5. The partial products are formed in register C||A||Q.
6. Each multiplier (Q) bit, beginning with the LSB, is processed (if bit is 1, B is added to partial product of A; if bit is 0, do nothing)
7. C||A||Q is shifted right using the shift register
 - Partial product bits fill vacant locations in Q as multiplier is shifted out
 - If overflow during addition, the outgoing carry is recovered from C during the right shift
8. Steps 6 and 7 are repeated until $P = 0$ as detected by Zero detect.

Multiplier Example: ASM Chart

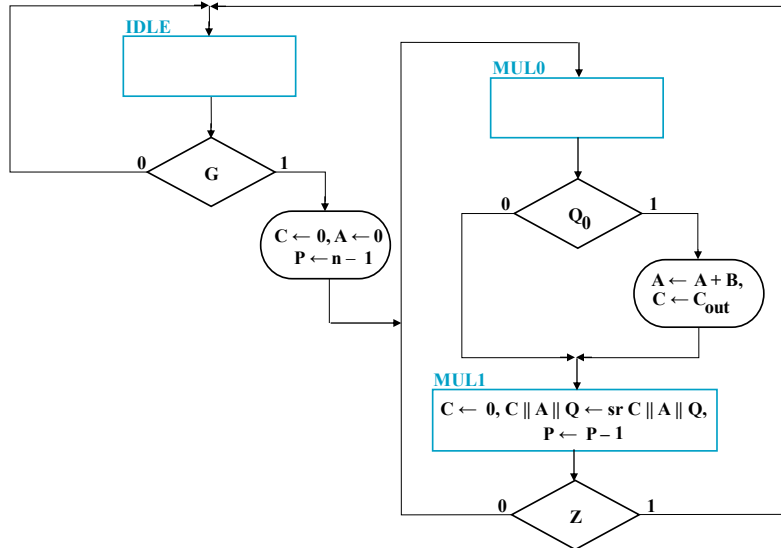

7

Multiplier Example: ASM Chart (Contd.)


- Three states are necessary to implement multiplier
 - IDLE state:
 - Input **G** is used as the condition for starting the multiplication
 - **C**, **A**, and **P** are initialized
 - MUL0 state: conditional addition is performed based on the value of **Q₀**.
 - MUL1 state:
 - Right shift is performed to capture the partial product and position the next bit of the multiplier in **Q₀**
 - Down counter $P = P - 1$
 - $P=0$ is used to sense completion or continuation of the multiplication.

Control and sequencing

- The ASM chart provides information about
 - **Control** of the microoperations (control word)
 - **Sequencing** of these operations
- The design can be split up in two parts:
 - Control signals
 - Sequencing

9

Control signals for multiplier

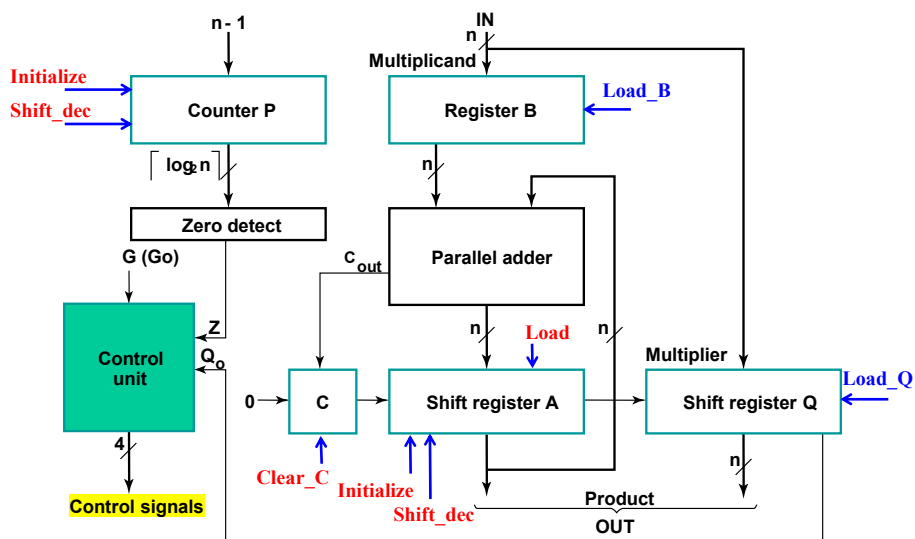

10

Multiplier Example: Control Signal Table

Control Signals for Binary Multiplier

Block diagram module	Microoperation	Control signal name	Control signal expression
Register A :	$A \leftarrow 0$	Initialize	IDLE · G
	$A \leftarrow A + B$	Load	MUL0 · Q_0
	$C \parallel A \parallel Q \leftarrow sr C \parallel A \parallel Q$	Shift_dec	MUL1
Register B :	$B \leftarrow IN$	Load_B	LOADB
Flip-Flop C :	$C \leftarrow 0$	Clear_C	IDLE · $G + MUL1$
	$C \leftarrow C_{out}$	Load	—
Register Q :	$Q \leftarrow IN$	Load_Q	LOADQ
	$C \parallel A \parallel Q \leftarrow sr C \parallel A \parallel Q$	Shift_dec	—
Counter P :	$P \leftarrow n - 1$	Initialize	—
	$P \leftarrow P - 1$	Shift_dec	—

11


Multiplier Example: Control Signal Table (Contd.)

- Signals are defined on a register basis
- LOAD_Q and LOAD_B: external signals controlled from the system using the multiplier and will not be considered a part of this design
- Some control signals are “reused” for different registers.
 - Four control signals are the “outputs” of the control unit:
initialize, load, shift_dec, clear_c

12

Multiplier Example – Sequencing part of ASM

 - With the outputs represented by the table, they can be removed from the ASM making the ASM to represent only the sequencing (next state) behavior → Simplified ASM chart. Similar to a state diagram/graph but without outputs specified.



13

Overview

- Control and Sequencing
 - Algorithmic State Machine (ASM) Chart of Multiplier
 - Hardwired control
 - Microprogrammed control

14

Control

- **Hardwired Control**
 - Implemented using gates and flip-flops
 - Faster, less flexible, limited complexity
- **Microprogram Control**
 - Control Store
 - Memory storing control signals and next state info
 - Controller sequences through memory
 - Slower, more flexible, greater complexity

15


Hardwired control

- **Control Design Methods**
 - (1) Sequential circuit techniques; studied earlier in this course
 - Procedure specializations that use a single signal to represent each state
 - (2) Sequence Register and Decoder
 - Sequence register with encoded states, e.g., 00, 01, 10, 11.
 - Decoder outputs produce “state” signals, e.g., 0001, 0010, 0100, 1000.
 - (3) One Flip-Flop per State
 - Flip-flop outputs as “state” signals, e. g., 0001, 0010, 0100, 1000.

16

 (2) Sequencer (sequence register) and Decoder

- Use a register to represent the states and a decoder to generate an output signal corresponding to each state
- Use the State Table to find the input logic



17

Multiplier Example: Sequencer and Decoder Design - Specification

- Define:
 - States: IDLE, MUL0, MUL1
 - Input Signals: G, Z, Q₀ (Q₀ affects outputs, not next state)
 - Output Signals: Initialize, Load, Shift_Dec, Clear_C
 - State Transition Diagram (Use Sequencing ASM)
 - Output Function: Use Control Signal Table
 - Decide on type of flip-flops to use
- Find:
 - State Assignments
 - Use two state bits to encode the three states IDLE, MUL0, and MUL1.

State	M1	M0
IDLE	0	0
MUL0	0	1
MUL1	1	0
Unused	1	1

18

Multiplier Example: Sequencer and Decoder Design - Formulation

- Assuming that state variables M1 and M0 are decoded into states, the next state part of the State Table is:

Current State	Input G Z	Next State M1 M0	Current State	Input G Z	Next State M1 M0
IDLE	0 0	0 0	MUL1	0 0	0 1
IDLE	0 1	0 0	MUL1	0 1	0 0
IDLE	1 0	0 1	MUL1	1 0	0 1
IDLE	1 1	0 1	MUL1	1 1	0 0
MUL0	0 0	1 0	Unused	0 0	d d
MUL0	0 1	1 0	Unused	0 1	d d
MUL0	1 0	1 0	Unused	1 0	d d
MUL0	1 1	1 0	Unused	1 1	d d

19

State Table with Decoder Outputs

Present State			Inputs		Next State		Decoder Outputs		
Name	M1	M0	G	Z	M1	M0	Idle	MUL0	MUL1
Idle	0	0	0	X	0	0	1	0	0
	0	0	1	X	0	1	1	0	0
MUL0	0	1	X	X	1	0	0	1	0
MUL1	1	0	X	0	0	1	0	0	1
	1	0	X	1	0	0	0	0	1
-	1	1	X	X	X	X	X	X	X
					D1	D0			

20

Multiplier Example: Sequencer and Decoder Design - Equations Derivation/Optimization

- Finding the equations for M_1 and M_0 using decoded states:

$$M_1 = MUL0$$

$$M_0 = IDLE \cdot G + MUL1 \cdot \bar{Z}$$
- The output equations using the decoded states:

$$Initialize = IDLE \cdot G$$

$$Load = MUL0 \cdot Q_0$$

$$Clear_C = IDLE \cdot G + MUL1$$

$$Shift_dec = MUL1$$
- Doing multiple level optimization, extract $IDLE \cdot G$:

$$START = IDLE \cdot G$$

$$M_1 = MUL0$$

$$M_0 = START + MUL1 \cdot \bar{Z}$$

$$Initialize = START$$


$$Load = MUL0 \cdot Q_0$$

$$Clear_C = START + MUL1$$

$$Shift_dec = MUL1$$
- The resulting circuit using flip-flops, a decoder, and the above equations is given on the next slide.

21

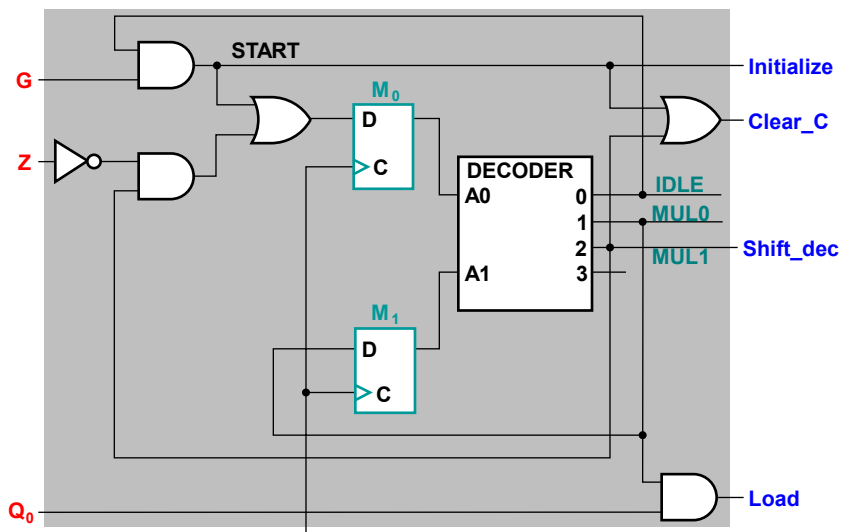Multiplier Example: Sequencer and Decoder Design - Implementation



22

```

--Binary multiplier with n=4
library ieee;
use ieee.std_logic_unsigned.all;

entity binary_multiplier is
  port(CLK, RESET, G, LOADB, LOADQ : in std_logic;
        MULT_IN : in std_logic_vector(3 downto 0);
        MULT_OUT : out std_logic_vector(7 downto 0));
end binary_multiplier;

architecture behavior_4 of binary_multiplier is
  type state_type is (IDLE, MUL0, MUL1);
  variable P := 3;
  signal state, next_state : state_type;
  signal A, B, Q : std_logic_vector(3 downto 0);
  signal C, Z : std_logic;
begin
  Z <= P(1) NOR P(0);
  MULT_OUT <= A & Q;

  state_register : process (CLK, RESET)
  begin
    if (RESET = '1') then
      state <= IDLE;
    elsif (CLK'event and CLK='1') then
      state <= next_state;
    end if;
  end process;

  next_state_func : process (G, Z, state)
  begin
    case state is
      when IDLE =>
        if G='1' then next_state <= MUL0;
        else next_state <= IDLE;
        end if;
      when MUL0 =>
        next_state <= MUL1;
      when MUL1 =>
        if Z='1' then next_state <= IDLE;
        else next_state <= MUL0;
        end if;
    end case;
  end process;

  datapath_func : process (CLK)
  variable CA : std_logic_vector(4 downto 0);
  begin
    if (CLK'event and CLK='1') then
      if LOADB='1' then
        B <= MULT_IN;
      end if;
      if LOADQ = '1' then
        Q <= MULT_IN;
      end if;

      case state is
        when IDLE =>
          if G = '1' then
            C <= '0';
            A <= "0000";
            P <= "11";
          end if;
        when MUL0 =>
          if Q(0)='1' then
            CA := ('0' & A) + ('0' & B);
          else
            CA := C & A;
          end if;
          C <= CA(4);
          A <= CA(3 downto 0);
        when MUL1 =>
          C <= '0';
          A <= C & A(3 downto 1);
          Q <= A(0) & Q(3 downto 1);
          P <= P - "01";
        end case;
      end if;
    end process;
  end behavior_4;

```

23

VHDL code: structural

- Homework assignment #5:
 - Write VHDL description of structural architecture similar to the structural description of the architecture from Example 2, Implementation 2 of Lab #4.
 - Create a testbench and simulate in Aldec-HDL.
 - Report should contain: title, name, brief description, VHDL code (with nice indentation and useful comments throughout the code), simulation waveforms (black on white and horizontal).
 - Report should be a single PDF file named "hw5_YourFirstName_YourLastName.pdf"


24

(3) One Flip-Flop per State

- This method uses one flip-flop per state and a simple set of transformation rules to implement the circuit.
- The design starts with the ASM chart, and replaces
 1. State Boxes with flip-flops,
 2. Scalar Decision Boxes with a demultiplexer with 2 outputs,
 3. Vector Decision Boxes with a (partial) demultiplexer,
 4. Junctions with an OR gate, and
 5. Conditional Outputs with AND gates.
- More flip-flops needed than in previous method


25

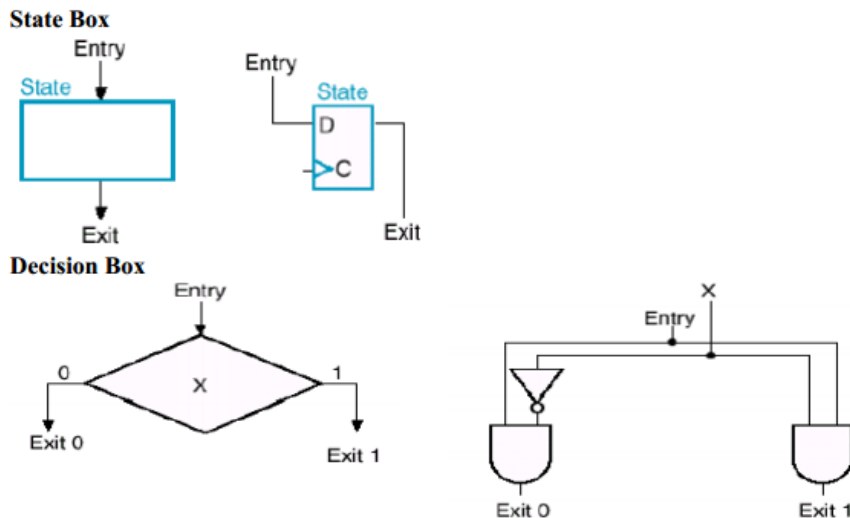State box and Scalar decision box transformations




Vector decision box transformation

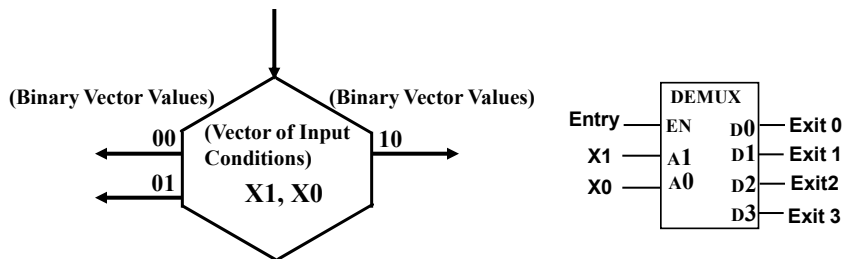- Each Decision box transforms to a Demultiplexer
- Entry point is Enable inputs
- The Conditions are the Select inputs
- Demultiplexer Outputs are the Exit points




Junction transformation, Conditional output box transformation


Junction

 

 Conditional output box: use the output of the decision box as control signal



Logic Diagram

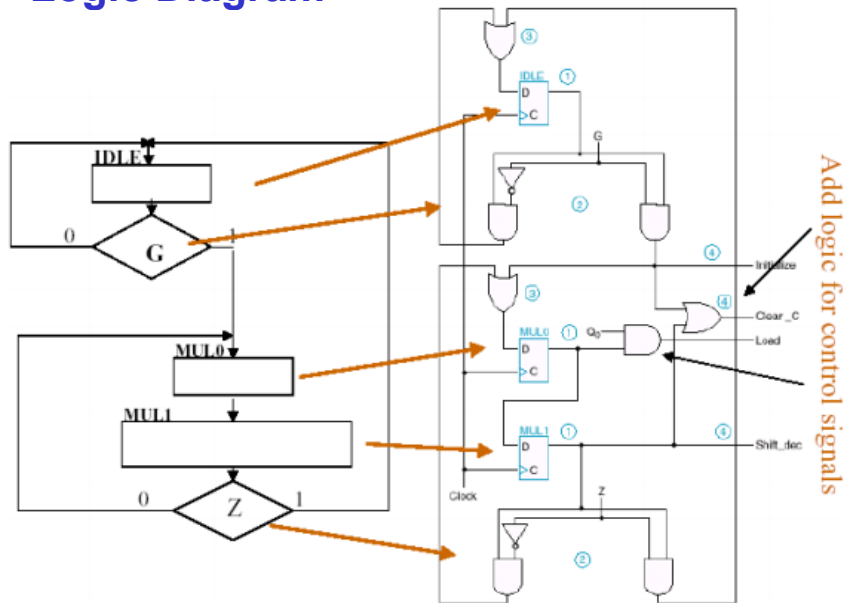


We assume that G is active for only one clock period.

Overview

- Control and Sequencing
 - Algorithmic State Machine (ASM) Chart of Multiplier
 - Hardwired control
 - **Microprogrammed control**

Datapath + Control unit/path

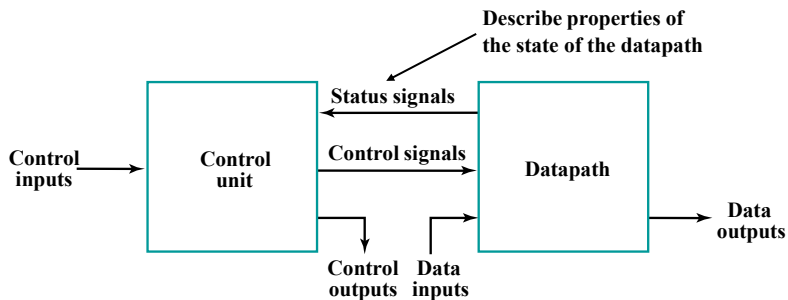
- Datapath - performs data transfer and processing operations
- Control unit/path - determines the enabling and sequencing of the operations



Datapath + Control unit/path

- Datapath:
 - Registers
 - MUXes, ALUs, Shifters, Combinational Circuits and Buses
 - Implements microoperations (under control of the control unit)
- Control unit:
 - Selects the microoperation
 - Determines the sequence (based on status and input signals)
 - Design:
 - State diagram or ASM
 - Microoperations
 - Sequence


Multiplier Example

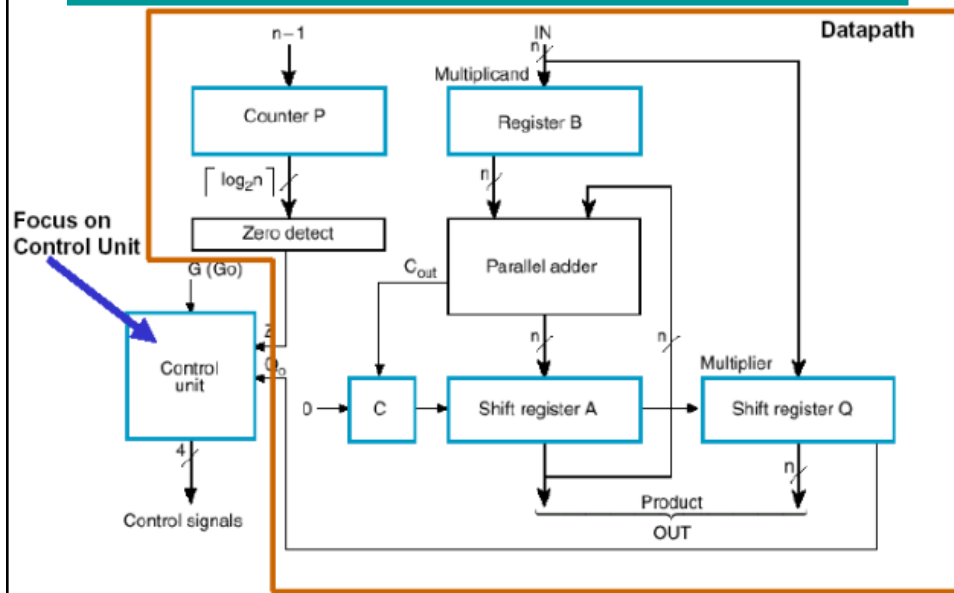

Microprogrammed Control

- Is a control unit whose control words are stored in memory, called control memory.
- A control word contains a **microinstruction** that specifies one or more **microoperations**.
- A sequence of microinstructions is called a **microprogram**.
- A microprogram is stored in ROM (thus fixed) or in RAM (called writable control memory).

Control Unit Organization

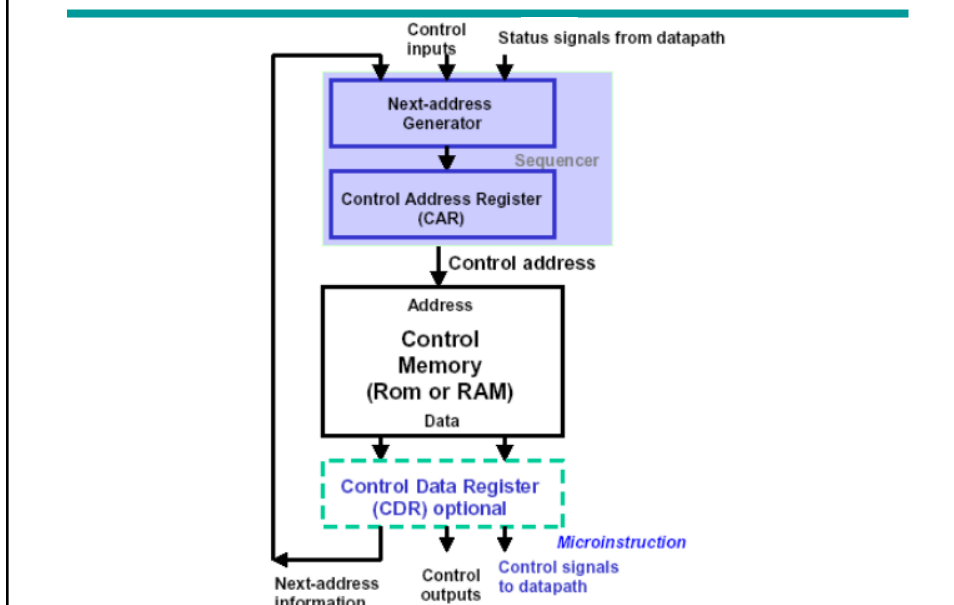

Microprogrammed Control

- The Control Data Register (CDR) is optional:
 - Allows higher clock frequencies (pipelining)
 - Makes the sequencing more complicated for decisions based on status bits
- If the CDR is omitted:
 - The only register in the control unit is the Control Address Register (CAR)
 - The memory and next-address generator are combinational
 - Thus the state of the control unit is given by the contents of the CAR
 - New control data will appear at the output of the memory as long as the address is applied


Microprogrammed Control

- The next address (determining the next instruction of the new state) is function of the next-address bits and the STATUS signals/bits.
- The way we designed the control unit, the status bits can only affect the next address (thus next state).
[note: status bits do not control the datapath directly]
- Thus status bits cannot directly affect the output or cause a register transfer operation (except by affecting the address).
- This means that the sequential circuit of the control unit must be a Moore type.

ASM of the Control Unit

- Moore type circuit:
 - No conditional output boxes allowed
 - Replace the conditional output boxes by states
 - Additional states are required for the same hardware algorithm
 - Also, only one decision box between states preferred (for simple next address generation)


ASM of the Control Unit

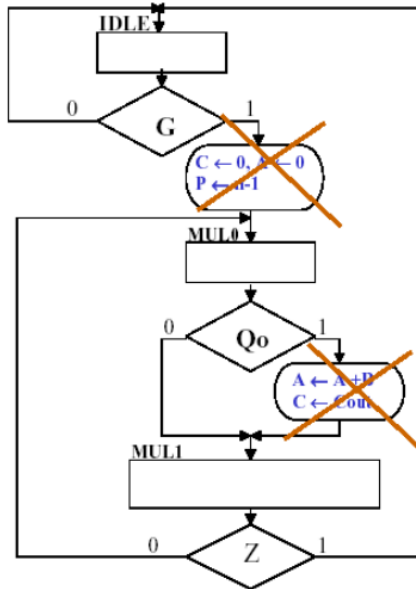

39

ASM of the Control Unit

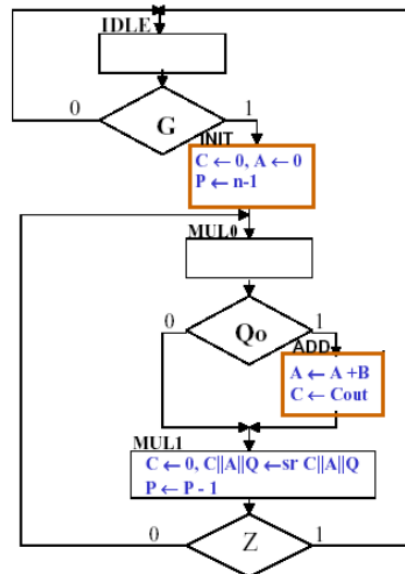- Two additional states: INIT, ADD
- Total of 5 states needed




Design of the Control Unit

- To design the (micro)sequencer for the multiplier and the microprogram we need to determine:
 - The bits in the control word
 - The size of the Control memory (ROM)
 - The size of the Control Address Register (CAR)
 - Next-address generator structure
- Control word
- Sequencer

Control Signals and Datapath

- Use the same Datapath:

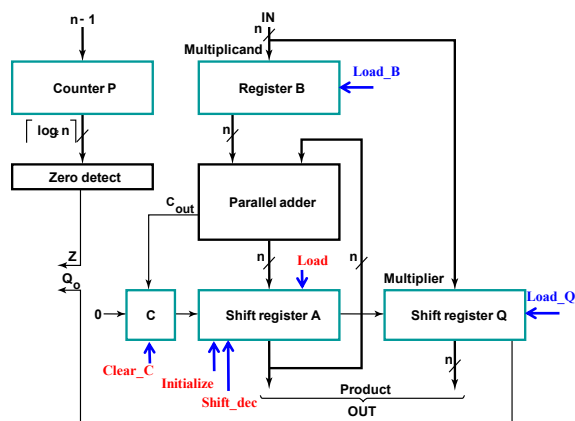

- We need four control signals:
 - Initialize
 - Load
 - Clear_C
 - Shift_Dec
- Status bits: Q_0 , Z

Control Signals and Register Transfers

- From the datapath and ASM one finds the **register transfers** initiated by the control signals.
- From the ASM one finds the **states in which the signals are active**


Control signal	Register transfers	States in which signal is active
Initialize	$A \leftarrow 0, P \leftarrow n-1$	INIT
Load	$A \leftarrow A + B, C \leftarrow C_{out}$	ADD
ClearC	$C \leftarrow 0$	INIT, MUL1
Shift/Dec	$C A Q \leftarrow srC A Q, P \leftarrow P-1$	MUL1

43

Control Signals, Control Word Format

- Four control signals needed.
- We can use these signals as is or encode them to reduce the number of bits needed in the control word.
- If we do not encode these: 4 bits needed
 - Initialize 0001
 - Load 0010
 - ClearC 0100
 - Shift/Dec 1000

Control Word Format

 

Determines the sequencing

4 bits for the control signals


44

Sequencer

- The **sequencing** is determined by the ASM chart
- First, determine the sequencing requirements:
 - IDLE: next state function of G
 - MUL0: next state function of Q₀
 - MUL1: next state function of Z
- We need a pair of addresses to direct to the next state depending on the values of the status or input signals
- SEL determines which next address to use

45

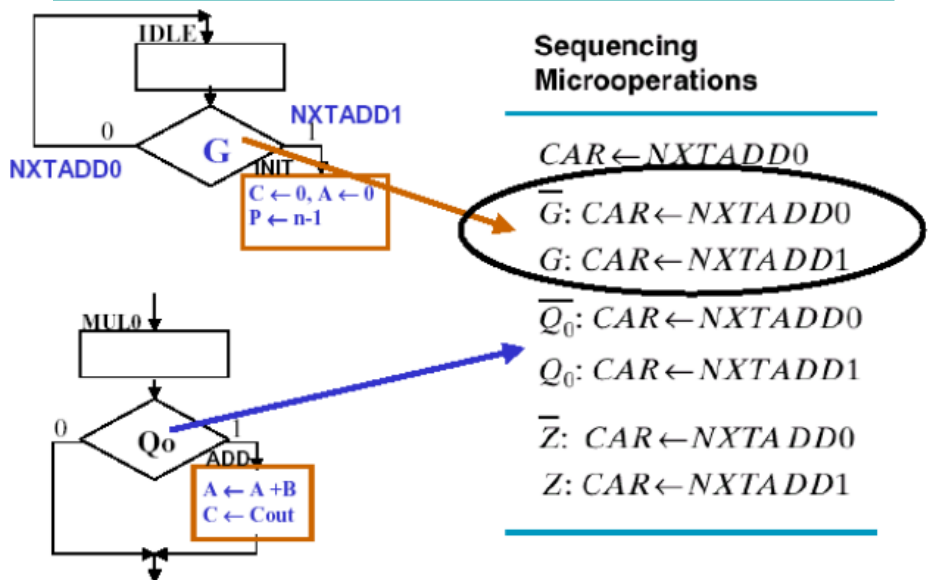Control Sequences for the micro operations based on decision boxes in the ASM chart:



SEL Field definition and Code in the Control Word

SEL Field Definition:		Sequencing Microoperations	
Symbolic notation	Binary Code		
NXT	00	$CAR \leftarrow NXTADD0$	
DG	01	$\overline{G}: CAR \leftarrow NXTADD0$ $G: CAR \leftarrow NXTADD1$	
DQ	10	$\overline{Q}_0: CAR \leftarrow NXTADD0$ $Q_0: CAR \leftarrow NXTADD1$	
DZ	11	$\overline{Z}: CAR \leftarrow NXTADD0$ $Z: CAR \leftarrow NXTADD1$	

11	9	8	6	5	4	3	0
NXTADD1		NXTADD0		SEL		DATAPATH	


↑

17

Design of Control Unit

- ROM size:
 - Word length: 12 bits (control word)
 - Size: 5 storage location, one for each state
- Address bits:
 - 3 bits to address 5 locations
 - CAR is 3 bits wide
- The address loaded in the CAR:
 - Comes from the next-address info in the microinstruction: NXTADD0 or NXTADD1

Microprogrammed Control Unit

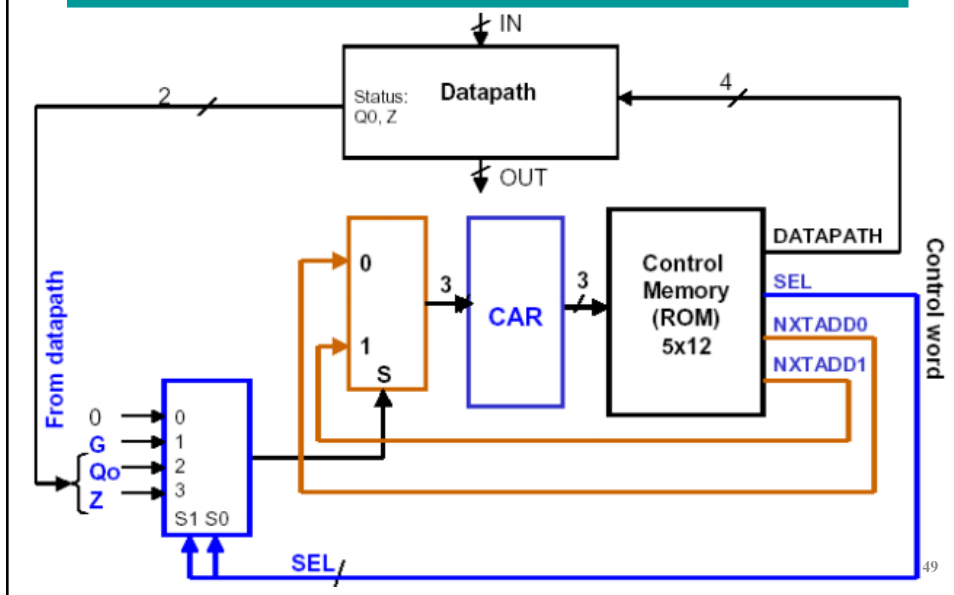

Register Transfer Description of the Microprogram

- Each memory location contains a microinstruction, to be executed in the corresponding state. The register transfer statements are:

Address	Symbolic transfer statement
IDLE	$G: CAR \leftarrow \text{INIT}, \bar{G}: CAR \leftarrow \text{IDLE}$
INIT	$C \leftarrow 0, A \leftarrow 0, P \leftarrow n-1, CAR \leftarrow \text{MUL0}$
MUL0	$Q_0: CAR \leftarrow \text{ADD}, \bar{Q}_0: CAR \leftarrow \text{MUL1}$
ADD	$A \leftarrow A + B, C \leftarrow C_{\text{out}}, CAR \leftarrow \text{MUL1}$
MUL1	$C \leftarrow 0, C[A]Q \leftarrow \text{sr } C[A]Q, Z: CAR \leftarrow \text{IDLE}, \bar{Z}: CAR \leftarrow \text{MUL0}, P \leftarrow P-1$


Symbolic Microprogram

- The above Register Transfer Operation can be translated into a symbolic microprogram (control words):

- Example:

address IDLE: $G: CAR \leftarrow INIT, \bar{G}: CAR \leftarrow IDLE$

Can be written as:

 

51


Symbolic Microprogram

Address	NXTADD1	NXTADD0	SEL	DATAPATH
IDLE	INIT	IDLE	DG	None
INIT	—	MUL0	NXT	IT, CC
MUL0	ADD	MUL1	DQ	None
ADD	—	MUL1	NXT	LD
MUL1	IDLE	MUL0	DZ	CC, SD

IDLE	$G: CAR \leftarrow INIT, \bar{G}: CAR \leftarrow IDLE$
INIT	$C \leftarrow 0, A \leftarrow 0, P \leftarrow n-1, CAR \leftarrow MUL0$
MUL0	$Q_0: CAR \leftarrow ADD, \bar{Q}_0: CAR \leftarrow MUL1$
ADD	$A \leftarrow A + B, C \leftarrow C_{out}, CAR \leftarrow MUL1$
MUL1	$C \leftarrow 0, C A Q \leftarrow sr C A Q, Z: CAR \leftarrow IDLE, \bar{Z}: CAR \leftarrow MUL0, P \leftarrow P-1$

52

Binary Microprogram

 

- Similar for the other instructions:

Address	NXTADD1	NXTADD0	SEL	DATAPATH	Address	NXTADD1	NXTADD0	SEL	DATAPATH
IDLE	INIT	IDLE	DG	None	000	001	000	01	0000
INIT	—	MUL0	NXT	IT, CC	001	000	010	00	0101
MUL0	ADD	MUL1	DQ	None	010	011	100	10	0000
ADD	—	MUL1	NXT	LD	011	000	100	00	0010
MUL1	IDLE	MUL0	DZ	CC, SD	100	000	010	11	1100

53

VHDL code

- Homework assignment #6:
 - Write VHDL structural description of this multiplier (slide #49) using the microprogrammed approach for the control unit.
 - Use a ROM as studied in Lab #5.
 - Create a testbench and simulate in Aldec-HDL.
 - Report should contain: title, name, brief description, VHDL code (with nice indentation and useful comments throughout the code), simulation waveforms (black on white and horizontal).
 - Report should be a single PDF file named "hw6_YourFirstName_YourLastName.pdf"

54

Summary

- Interaction between datapaths and control units
- Two types of control units:
 - Non-programmed
 - Programmed
- Two implementation approaches for Hardwired Control (non-programmed):
 - Sequence Register and Decoder
 - One Flip-Flop per state
- Use of ASM to specify control functions:
 - Microoperations
 - Sequence of operations
- Microprogrammed control is a more structured approach for complex systems

55

Appendix A: Speeding Up the Multiplier

- In processing each bit of the multiplier, the circuit visits states MUL0 and MUL1 in sequence.
- By redesigning the multiplier, is it possible to visit only a single state per bit processed?

56

Speeding Up Multiply (Contd.)

- The operations in MUL0 and MUL1:
 - In MUL0, a conditional add of B
 - In MUL1, a right shift of $C \parallel A \parallel Q$ in a shift register, the decrementing of P, and a test for $P = 0$ (on the old value of P)

- Any solution that uses one state must combine all of the operations listed into one state
 - The operations involving P are already done in a single state, so not a problem.
 - The right shift, however, depends on the result of the conditional addition. So these two operations must be combined!


57

Speeding Up Multiply (Contd.)

- By replacing the shift register with a combinational shifter and combining the adder and shifter, the states can be merged.

- The C-bit is no longer needed.

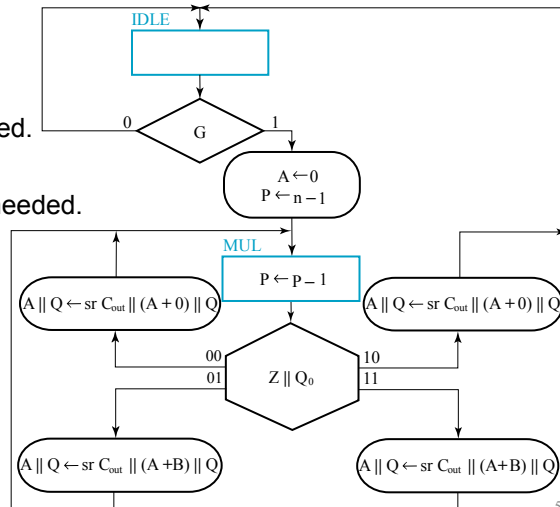- In this case, Z and Q_0 have been made into a vector.



58