

EE 459/500 – HDL Based Digital Design with Programmable Logic

Lecture 15 Memories

1

Overview

- Introduction
- Memories
 - Read Only Memories
 - Random Access Memories
 - FIFOs

2

Motivation

- Most applications need memory!
- Store constants (filter coefficients), implement instruction and data, LUTs, FIFOs, registers, etc.
- FPGAs incorporate dedicated memories to eliminate the need to interface with external memory chips

3

Memories

- The good news: huge selection of technologies
 - Small & faster vs. large & slower
 - Every year capacities go up and prices go down
 - New kid on the block: high density, fast flash memories
 - Non-volatile, read/write, no moving parts! (robust, efficient)
- The bad news: perennial system bottleneck
 - Latencies (access time) haven't kept pace with cycle times
 - Separate technology from logic, so must communicate between silicon; physical limitations (# of pins, R's, C's, and L's) limit bandwidths
 - New hopes: optical interconnect, 3D IC's
 - Likely the limiting factor in cost & performance of many digital systems: designers spend a lot of time figuring out how to keep memories running at peak bandwidth

4

Memories classification


Read-Write Memory			Read-Only Memory
Volatile Memory		Non-volatile Memory	Mask-Programmed ROM (PROM) (nonvolatile)
Random Access	Sequential Access	EPROM EEPROM FLASH	
SRAM DRAM	FIFO LIFO Shift Register CAM		

- Volatile: need electrical power
- Nonvolatile: magnetic disk, retains its stored information after the removal of power
- Random access: memory locations can be read or written in a random order
- EPROM: erasable programmable read-only memory
- EEPROM: electrically erasable programmable read-only memory
- FLASH: memory stick, USB disk
- Access pattern: sequential access: (video memory streaming) first-in-first-out (buffer), last-in-first-out (stack), shift register, content-addressable memory
- Static vs. Dynamic: dynamic needs periodic refresh but is simpler, higher density
- **Key Design Metrics:**
 1. Memory Density (number of bits/mm²) and Size
 2. Access Time (time to read or write) and Throughput
 3. Power Dissipation

5


Basic memory system

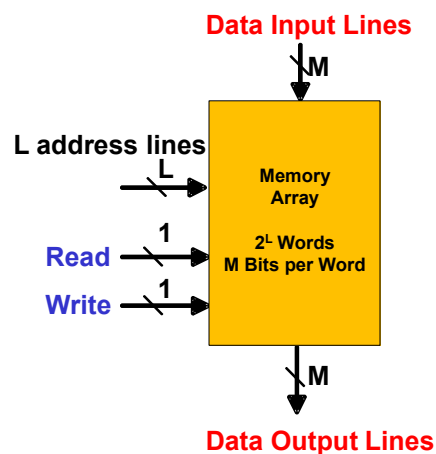- L address lines are decoded to address 2^L **words** of memory
- Each word is **M bits**
- **Read** and **Write** are single control lines defining the simplest memory operations




6

Memory Array Architecture

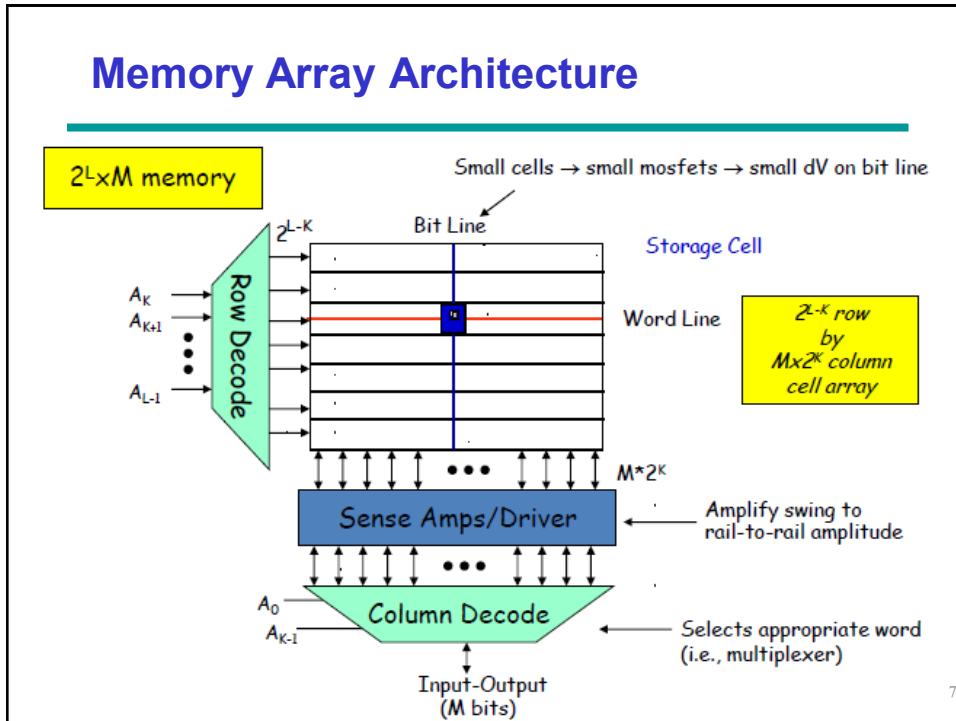


Memory Operation Timing - Read

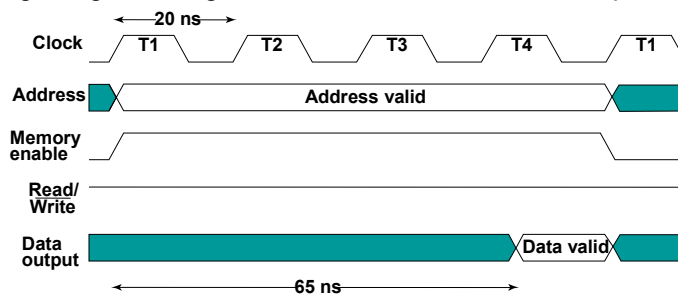- Most basic memories are **asynchronous**
 - Storage in latches/flip-flops or electrical charge storage elements (C's)
 - No clock**
 - Controlled by control inputs and address, which are controlled by CPU and **synchronized** by its own clock
- Timing of signal changes/data observation is critical to operation



- Read cycle:** the **access time**, the maximum time from the application of the address to the appearance of the data at the Data output

Memory Operation Timing - Write

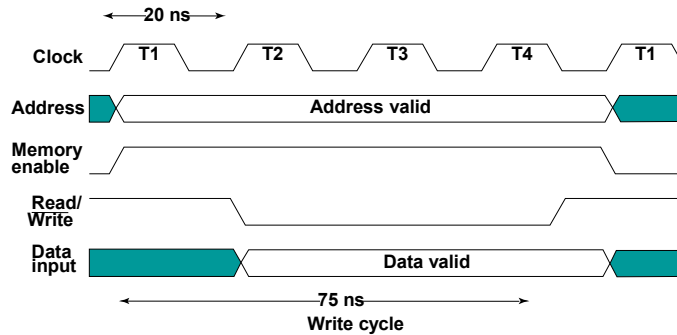

- **Write cycle:** the maximum time from the application of the address to the completion of all internal operations required to store a word
- Critical times measured with respect to edges of write pulse (1-0-1):
 - Address must be established at least a specified time before 1-0 and held for at least a specified time after 0-1 to avoid disturbing stored contents of other addresses
 - Data must be established at least a specified time before 0-1 and held for at least a specified time after 0-1 to write correctly

9

Overview

- Motivation
- Memories
 - Read Only Memories
 - Random Access Memories
 - FIFOs

10

Read Only Memories (ROMs)

- ROM modeling: ROMs are usually modeled in VHDL with an array of array object
- Signal-Based Declaration VHDL Coding Example

```
type rom_type is array (0 to 127) of std_logic_vector (19 downto 0);
signal ROM : rom_type:= (
    X"0200A", X"00300", X"08101", X"04000", X"08601", X"0233A", X"00300", X"08602",
    X"02310", X"0203B", X"08300", X"04002", X"08201", X"00500", X"04001", X"02500",
    (...)
    X"04078", X"01110", X"02500", X"02500", X"0030D", X"02341", X"08201", X"0410D"
);
```

Arrays in VHDL

- `type` WORD16 is array (15 downto 0) of bit;
- `signal` DATA_WORD: WORD16; -- a 16-bit register
- `subtype` WORD8 is STD_LOGIC_VECTOR (7 downto 0);
- `type` TAB12 is array (11 downto 0) of WORD8;
- `type` TAB03 is array (2 downto 0) of TAB12;
- You can also declare an array as a matrix:
- `subtype` TAB13 is array (7 downto 0, 4 downto 0) of STD_LOGIC_VECTOR (8 downto 0);

Examples

- **subtype** WORD8 is STD_LOGIC_VECTOR (7 downto 0);
- **type** TAB05 is array (4 downto 0) of WORD8;
- **type** TAB03 is array (2 downto 0) of TAB05;
- **signal** WORD_A : WORD8;

- **signal** TAB_A, TAB_B : TAB05;
- **signal** TAB_C, TAB_D : TAB03;
- **constant** CNST_A : TAB03 := (
 ("00000000","01000001","01000010","10000011","00001100"),
 ("00100000","00100001","00101010","10100011","00101100"),
 ("01000010","01000010","01000100","01000111","01000100"));
- TAB_A <= TAB_B; TAB_C <= TAB_D; TAB_C <= CNST_A;
- TAB_A (5) <= WORD_A; TAB_C (1) <= TAB_A;
- TAB_A (5) (0) <= '1'; TAB_C (2) (5) (0) <= '0';
- TAB_A (4 downto 1) <= TAB_B (3 downto 0);

13

Describing ROM with a Case Statement

```
ENTITY rom8x4 IS
  PORT (
    addr: in std_logic_vector(2 downto 0);
    q: out std_logic_vector(3 downto 0));
END rom8x4;

ARCHITECTURE behav OF rom8x4 IS
BEGIN

  PROCESS(addr)
  BEGIN
    CASE addr IS
      when "000" => q <= "0001";
      when "001" => q <= "0000";
      when "010" => q <= "0111";
      when "011" => q <= "1101";
      when "100" => q <= "1000";
      when "101" => q <= "1100";
      when "110" => q <= "0110";
      when "111" => q <= "1011";
      when others => NULL;
    END case;
  END process;
END behav;
```

14

ROMs in Xilinx Library

- **Spartan-6** library does not contain direct support for ROMs. However, block RAMs could be utilized.
 - http://www.xilinx.com/support/documentation/sw_manuals/xilinx11/spartan6_hdl.pdf
 - Atlys board has a Spartan-6 FPGA
- Virtex family of FPGAs do have library support for ROMs
- Example: **Virtex-4**:
 - http://www.xilinx.com/support/documentation/sw_manuals/xilinx11/virtex4_hdl.pdf
 - ROM16x1 (16-word by 1 bit ROM)
 - ROM32x1
 - ROM64x1
 - ROM128x1
 - ROM256x1...

15


Example: ROM16x1

```
library UNISIM;
use UNISIM.vcomponents.all;

-- ROM16X1: 16 x 1 Asynchronous Distributed => LUT ROM
-- Xilinx HDL Libraries Guide, version 11.2

ROM16X1_inst : ROM16X1
generic map (
  INIT => X"0000")
port map (
  O => O, -- ROM output
  A0 => A0, -- ROM address[0]
  A1 => A1, -- ROM address[1]
  A2 => A2, -- ROM address[2]
  A3 => A3 -- ROM address[3]
);

-- End of ROM16X1_inst instantiation
```

 

16

How do we use ROMs

```
architecture beh of my_example_rom is

    signal ABUS : std_logic_vector(3 downto 0);
    signal DBUS : std_logic_vector(1 downto 0);

begin

    bit0 : ROM16X1
        generic map (INIT => "1010 1110 0001 0001" )
        port map (O => DBUS(0), A0 => ABUS(0),
            A1 => ABUS(1), A2 => ABUS(2), A3 => ABUS(3) );
    bit1 : ROM16X1
        generic map (INIT => "1101 1010 1111 0101")
        port map (O => DBUS(1), A0 => ABUS(0),
            A1 => ABUS(1), A2 => ABUS(2), A3 => ABUS(3) );

    rom_inc : process(CLK) is
        begin
            if (CLK'event and CLK='1') then
                ABUS <= ABUS + 1;
            end if;
        end process;

    jump : process(DBUS) is
        begin
            if (DBUS="11") then
                ABUS <= "0000";
            end if;
        end;

end architecture;
```

17

Overview

- Motivation
- Memories
 - Read Only Memories
 - Random Access Memories
 - FIFOs

18


Random Access Memories (RAMs)

- Read/Write memory
- Types:
 - **Static RAM (SRAM):**
 - Once a word is written at a location, it remains stored as long as power is applied to the chip, unless the same location is written again.
 - **Fast speed**, but **their cost per bit higher**.
 - Application: Cache (\$) memories in Microprocessors
 - **Dynamic RAM (DRAM):**
 - The data stored at each location must be periodically refreshed by reading it and then writing it back again, otherwise it disappears.
 - **Their density is greater and their cost per bit lower**, but the **speed is slower**.


19

Static RAMs: Latch Based Memory

Set Reset Flip Flop

 

Register Memory

 


- Works fine for small memory blocks (e.g., small reg. files)
 - Inefficient in area for large memories
 - Density is the key metric in large memory circuits

How do we minimize cell size?

20

Static RAM Cell


6-Transistor SRAM Cell

 


- **Read:**
 1. Select row
 2. Cell pulls one line low and one high
 3. Sense output on bit and bit
- **Write:**
 1. Drive bit lines (e.g. bit=1, $\overline{\text{bit}}=0$)
 2. Select row
- **Why does this work?**
 - When one bit-line is low, it will force output high; that will set new state

21

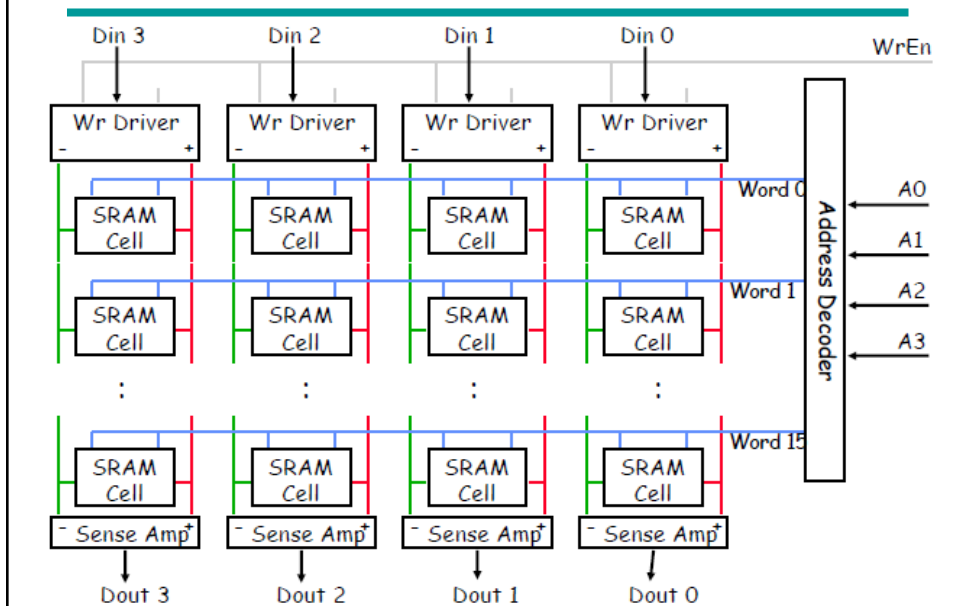Typical SRAM Organization: 16-word x 4-bit




Logic Diagram of a Typical SRAM

 


- Write Enable is usually active low (WE_L)
- Din and Dout are combined to save pins:
- A new control signal, Output Enable (OE_L)
 - WE_L is asserted (Low), OE_L is unasserted (High)
 - D serves as the data input pin
 - WE_L is unasserted (High), OE_L is asserted (Low)
 - D is the data output pin
 - Neither WE_L and OE_L are asserted?
 - Chip is disconnected
 - Never both asserted!

Typical SRAM Timing

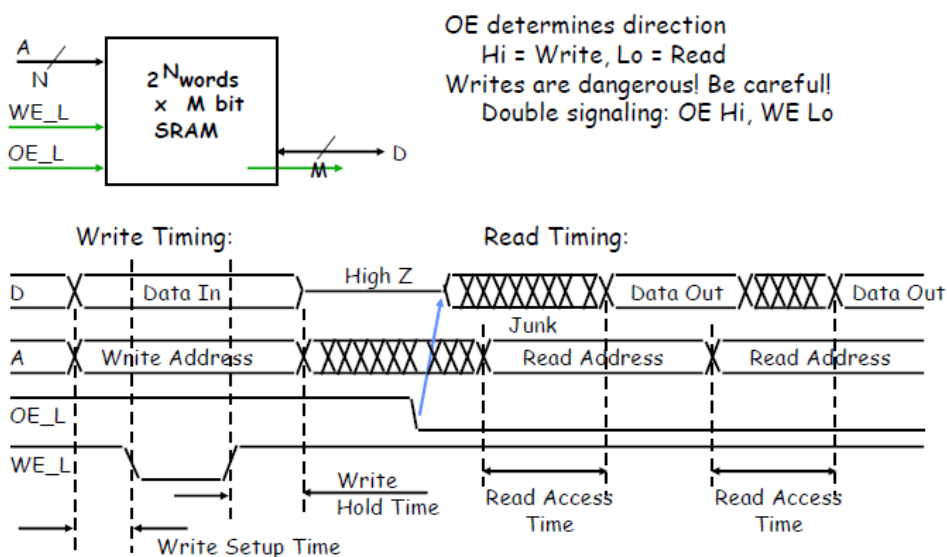

Making Larger Memories

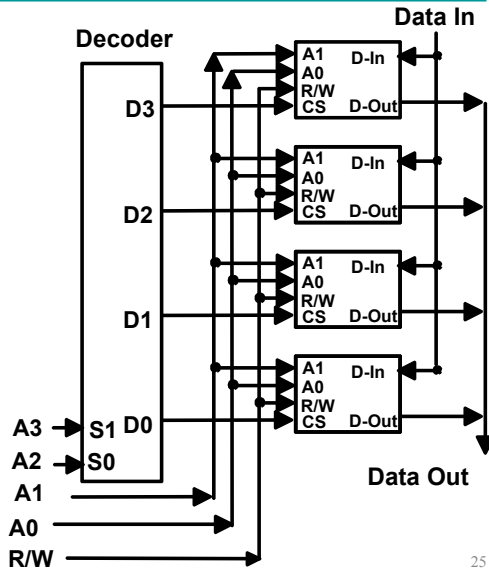
- We can make larger memories from smaller ones by using the decoded higher order address bits to control CS (chip select) lines, tying all address, data, and R/W lines in parallel
- A 16-Word by 1-Bit memory constructed using 4-Word by 1-Bit memory



25

Making Wider Memories

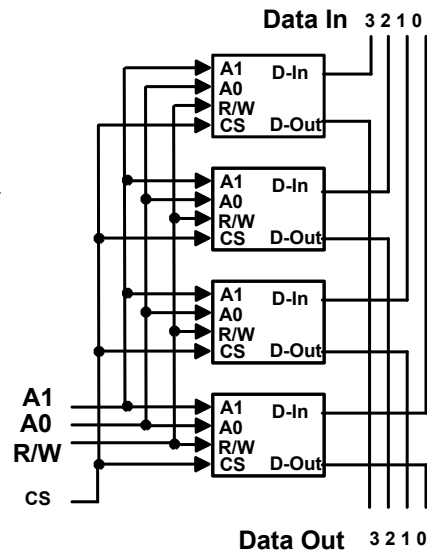- Tie the address and control lines in parallel and keep the data lines separate
- Example: make a 4-word by 4-bit memory from 4, 4-word by 1-bit memories
- Note: Both 16x1 and 4x4 memories take 4-chips and hold 16 bits of data



26

RAMs in Xilinx Library

- Static Block RAMs
 - Single port
 - RAM32X1S, RAM64X1S, ...
 - Dual port
 - RAM64X1D, RAM128X1D, ...
-
- The difference between single port RAM and dual port RAM is that single port RAM can be accessed at one address at one time, thus you can read/write only one memory cell during each clock cycle. Dual port RAM has ability to simultaneously read and write different memory cells at different addresses.
 - Single port uses a 6 transistor basic RAM cell, while the dual port RAM cell uses 8 transistor cell for memory.

27

Block RAMs (BRAMs)

- A **Block RAM** is a dedicated (cannot be used to implement other functions like digital logic) two port memory
- The Block RAM in **Spartan-6** FPGAs stores up to 18K bits of data and can be configured as:
 - Two independent 9 Kb RAMs
 - One 18 Kb RAM
- Write and Read are synchronous operations
- The two ports are symmetrical and totally independent, sharing only the stored data.
- Embedded dual- or single-port RAM modules, ROM modules, synchronous FIFOs, and data-width converters are easily implemented using the Xilinx CORE Generator block memory modules


28

Difference between Distributed and Block RAMs

- Distributed RAM = parallel array of large # of elements
→ distributed RAM is ideal for small sized memories.
For large memories, extra wiring delays
- Use block RAM for large sized memories and distributed RAM for small sized memories or FIFO's
- WRITE operation is synchronous in both
- READ operation:
 - Distributed RAM: asynchronous (data is read from memory as soon as the address is given, doesn't wait for the clock edge)
 - Block RAM: synchronous

 Example: RAM32X1S

```
library UNISIM;  
use UNISIM.vcomponents.all;  
  
-- RAM32X1S: 32 x 1 posedge write distributed => LUT RAM  
-- All FPGA  
-- Xilinx HDL Libraries Guide, version 11.2  
  
RAM32X1S_inst : RAM32X1S  
generic map (  
    INIT => X"00000000")  
port map (  
    O => O, -- RAM output  
    A0 => A0, -- RAM address[0] input  
    A1 => A1, -- RAM address[1] input  
    A2 => A2, -- RAM address[2] input  
    A3 => A3, -- RAM address[3] input  
    A4 => A4, -- RAM address[4] input  
    D => D, -- RAM data input  
    WCLK => WCLK, -- Write clock input  
    WE => WE -- Write enable input  
);  
-- End of RAM32X1S_inst instantiation
```



30

True dual-port 18 Kb block RAM dual-port memories

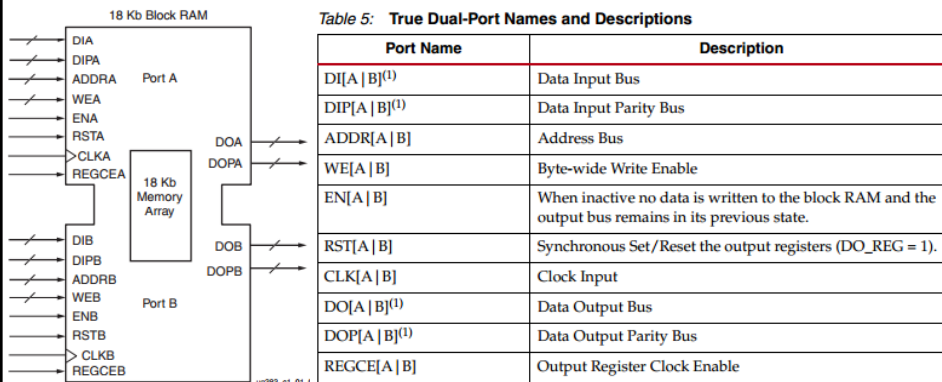


Table 5: True Dual-Port Names and Descriptions

Port Name	Description
DI[A B] ⁽¹⁾	Data Input Bus
DIP[A B] ⁽¹⁾	Data Input Parity Bus
ADDR[A B]	Address Bus
WE[A B]	Byte-wide Write Enable
EN[A B]	When inactive no data is written to the block RAM and the output bus remains in its previous state.
RST[A B]	Synchronous Set/Reset the output registers (DO_REG = 1).
CLK[A B]	Clock Input
DO[A B] ⁽¹⁾	Data Output Bus
DOP[A B] ⁽¹⁾	Data Output Parity Bus
REGCE[A B]	Output Register Clock Enable

Figure 1: True Dual-Port Data Flows

- See “Spartan-6 FPGA Block RAM Resources” for timing diagrams
 - http://www.xilinx.com/support/documentation/user_guides/ug383.pdf
 - http://www.xilinx.com/support/documentation/data_sheets/ds160.pdf

31

How to tell XST which type of RAM you want to use?

- XST (Xilinx Synthesis Tool) may implement a declared RAM as either
 - block RAM
 - distributed RAM
- You can force the implementation style to use block RAM or distributed RAM resources
- Done using the `ram_style` constraint
- Before the `begin` statement in the architecture section:
 - attribute `ram_style`: string;
 - attribute `ram_style` of ram: signal is “distributed”;
 - Here ram is the signal name. Change “distributed” to “block” to force XST to use block RAM resources. Default value of the attribute `ram_style` is “auto”.

Example

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity ram_example is
port ( Clk      : in std_logic;
      address  : in integer;
      we       : in std_logic;
      data_i   : in std_logic_vector(7 downto 0);
      data_o   : out std_logic_vector(7 downto 0)
      );
end ram_example;


architecture Behavioral of ram_example is
--Declaration of type and signal of a 256 element RAM; each word is 8 bit wide.
type ram_t is array (0 to 255) of std_logic_vector(7 downto 0);
signal ram : ram_t := (others => (others => '0'));
attribute ram_style: string;
attribute ram_style of ram : signal is "distributed";
begin

--process for read and write operation.
PROCESS(Clk)
BEGIN
    if(rising_edge(Clk)) then
        if(we='1') then
            ram(address) <= data_i;
        end if;
        data_o <= ram(address);
    end if;
END PROCESS;
end Behavioral;
```

Block RAM Applications

- The **Xilinx CORE Generator** program offers an easy way to generate wider and deeper memory structures using multiple Block RAM instances
- It outputs VHDL or Verilog instantiation templates and simulation models
- See Lab#5 for details

Creating BRAMs with Core Generator

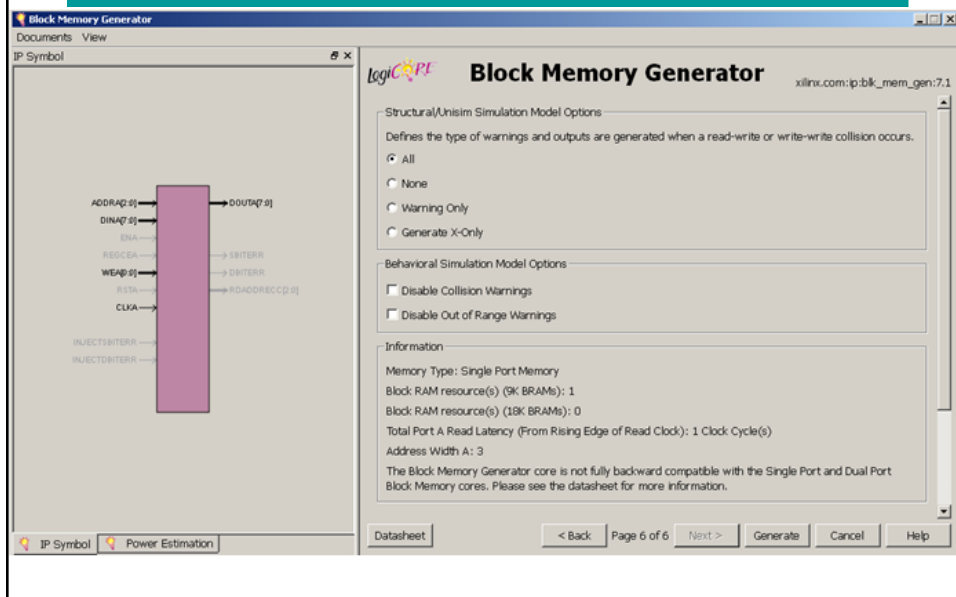

Using the result in your VHDL project

```
ENTITY my_bram8x8 IS
  PORT (
    clka : IN STD_LOGIC;
    wea  : IN STD_LOGIC_VECTOR(0 DOWNTO 0);
    addr : IN STD_LOGIC_VECTOR(2 DOWNTO 0);
    dina : IN STD_LOGIC_VECTOR(7 DOWNTO 0);
    douta : OUT STD_LOGIC_VECTOR(7 DOWNTO 0)
  );
END my_bram8x8;
```

- Use to instantiate components:

```
memory2 : my_bram8x8 port map (clka=>clk_1Hz, wea=>wea_null,
  addr=>my_addr_counter, dina=>dina_null,
  douta=>dout_bram8x8);
```

.coe file format (used during Core Generator usage)

```
memory_initialization_radix=2;
memory_initialization_vector=
10000000,
01000000,
00100000,
00010000,
00001000,
00000100,
00000010,
00000001;
```

Dynamic RAM (DRAM)


- Basic Principle: Storage of information on capacitors
- Charge and discharge of capacitor to change stored value
- Use of transistor as “switch” to:
 - Store charges
 - Charge or discharge
- You will normally not find DRAMs in FPGAs

Overview


- Motivation
- Memories
 - Read Only Memories
 - Random Access Memories
 - FIFOs




First-in-first-out (FIFO) Memory

- Used to implement *queues*.
- These find common use in computers and communication circuits.
- Generally, used for rate matching data producer and consumer:
 - Producer can perform many writes without consumer performing any reads (or vice versa). However, because of finite buffer size, on average, need equal number of reads and writes.
 - Typical uses:
 - Interfacing I/O devices. Example network interface. Data bursts from network, then processor bursts to memory buffer (or reads one word at a time from interface). Operations not synchronized.
 - Example: Audio output. Processor produces output samples in bursts (during process swap-in time). Audio DAC clocks it out at constant sample rate.

 

FIFO Interfaces

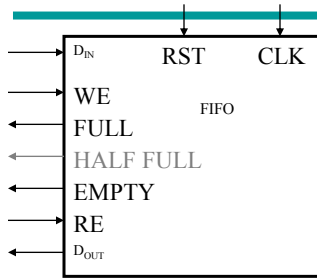

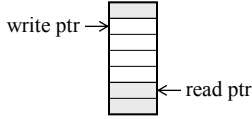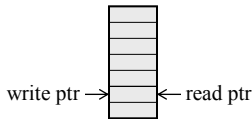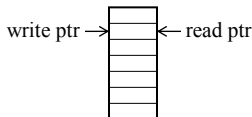- Address pointers are used internally to keep next write position and next read position into a dual-port memory.
 
 - If pointers equal after write \Rightarrow FULL:
 
 - If pointers equal after read \Rightarrow EMPTY:
 
- After write or read operation, FULL and EMPTY indicate status of buffer.
 - Used by external logic to control own reading from or writing to the buffer.
 - FIFO resets to EMPTY state.
 - HALF FULL (or other indicator of partial fullness) is optional.

41

FIFO Implementation

- Assume, dual-port memory with asynchronous read, synchronous write.
- Binary counter for each of read and write address. CEs controlled by WE and RE.
- Equal comparator to see when pointers match.
- Flip-flop each for FULL and EMPTY flags:

WE	RE	equal	$EMPTY_i$	$FULL_i$
0	0	0	0	0
0	0	1	$EMPTY_{i-1}$	$FULL_{i-1}$
0	1	0	0	0
0	1	1	1	0
1	0	0	0	0
1	0	1	0	1
1	1	0	0	0
1	1	1	$EMPTY_{i-1}$	$FULL_{i-1}$

- FIFOs available in Xilinx library for Virtex-4 and up devices
- For Spartan-6 one could use LogiCORE FIFO Generator?
- See Lab#7 supplemental

42

Summary

- Memories are complex circuits and different from random logic
- Companies, like Xilinx, offer pre-designed cores to help designers improve productivity
- Always consult documentation of FPGAs to see what types of memory blocks are available
- Do not underestimate FIFOs
- Timing issues are extremely important


References and Credits

- Textbook
 - Sections 3.2, 3.4, 6.6, 8.7, 8.8, and 11.2
- Chapter 13 of Volnei A. Pedroni book
- Chapter 9 of M. Morris Mano and Charles Kime book
- Jan Rabaey book (on timing and clock issues)
- MIT 6.111 slides
 - <http://web.mit.edu/6.111/www/f2011/handouts/L10.pdf>
- Berkeley CS150 slides
 - <http://www-inst.eecs.berkeley.edu/~cs150/fa07/Lectures/lec13-mem-sram.pdf>
- XST User Guide for Virtex-6, Spartan-6, and 7 Series Devices - ROMs and ROM coding examples (page 247):
 - http://www.xilinx.com/support/documentation/sw_manuals/xilinx13_1/xst_v6s6.pdf
- Spartan-6 Libraries Guide for HDL Designs
 - http://www.xilinx.com/support/documentation/sw_manuals/xilinx11/spartan6_hdl.pdf
- Spartan-6 FPGA Block RAM Resources
 - http://www.xilinx.com/support/documentation/user_guides/ug383.pdf

Appendix A:

Revisiting Static RAM Cell: SR latch based

 
- Storage Cell
 - SR Latch
 - Select input for control
 - Dual Rail Data Inputs B and \overline{B}
 - Dual Rail Data Outputs C and \overline{C}



45


SRAM Bit Slice

 - Represents all circuitry that is required for 2^n 1-bit words
 - Multiple RAM cells
 - Control Lines:
 - Word select i – one for each word
 - Read/Write
 - Bit Select
 - Data Lines:
 - Data in
 - Data out



2ⁿ-Word by 1-Bit RAM IC

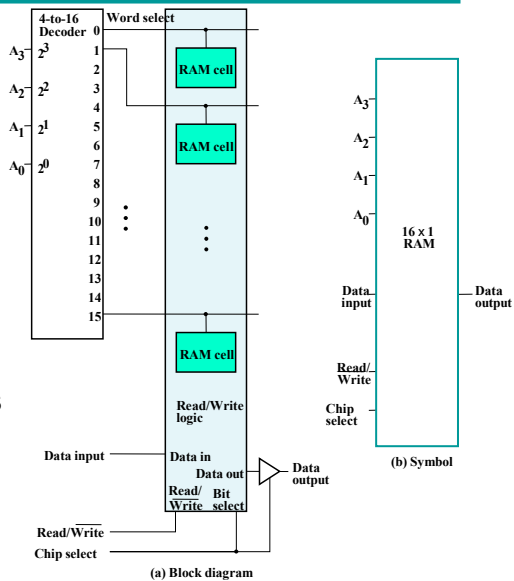- To build a RAM IC from a RAM slice:
 - Decoder decodes the n address lines to 2^n word select lines
 - A 3-state buffer on the data output permits RAM ICs to be combined into a RAM with $c \times 2^n$ words



Cell Arrays and Coincident Selection

- Memory arrays can be very large =>
 - Large decoders
 - Large fanouts for the input bit lines
 - The decoder size and fanouts can be reduced by approximately \sqrt{n} using a coincident selection in a 2-D array: uses two decoders, one for words and one for bits:
 - Word select becomes Row select
 - Bit select becomes Column select
- See next slide for example

