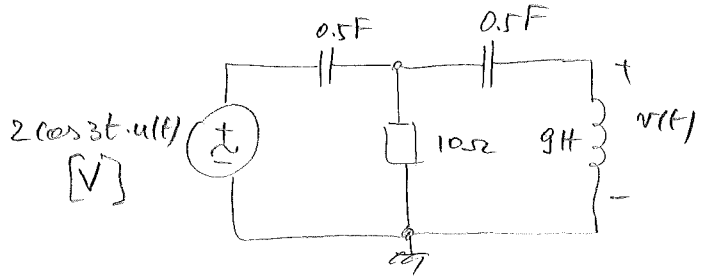




3 Source Transformations

Example 1: Use source transformations to find an expression for $v(t)$




Observe that there are no initial conditions!


⇓ Convert to frequency s-domain

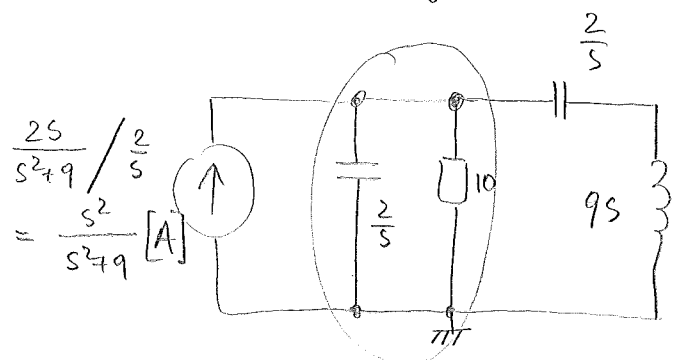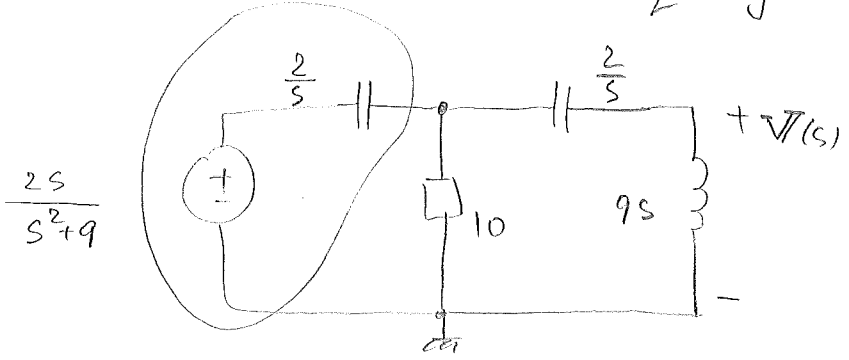

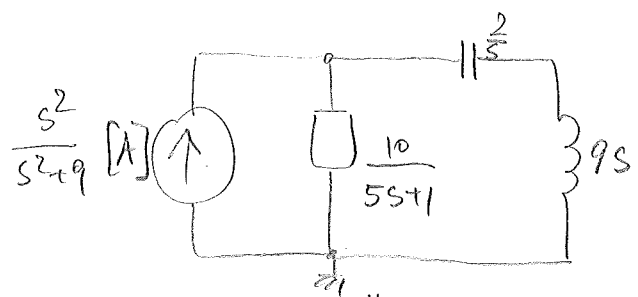
$$\Downarrow Z_1 = \frac{2}{s} \parallel 10 = \frac{\frac{20}{s}}{\frac{2}{s} + 10} = \frac{20}{10s + 2} = \frac{10}{5s + 1} \text{ [}\Omega\text{]}$$


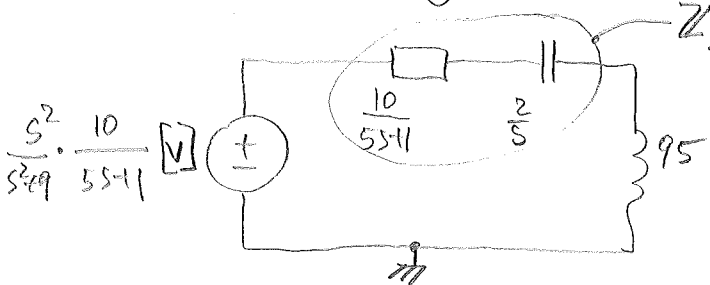
$$\Downarrow Z_2 = \frac{10}{5s + 1} + \frac{2}{s} = \frac{20s + 2}{s(5s + 1)} \text{ [}\Omega\text{]}$$



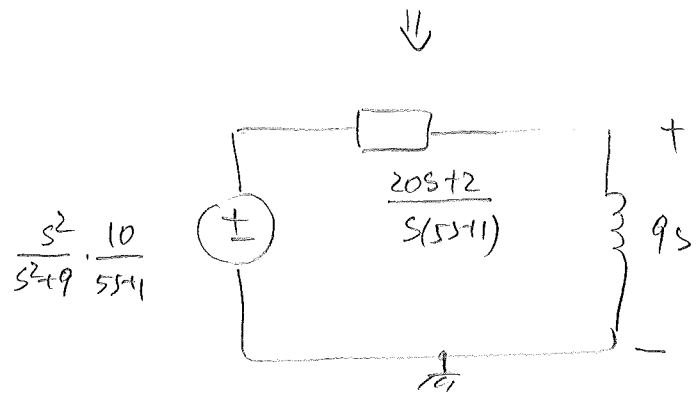

By voltage division:

$$V(s) = \frac{9s}{9s + \frac{20s+2}{s(5s+1)}} \times \frac{s^2}{s^2+9} \cdot \frac{10}{5s+1}$$

$$= \frac{180s^4}{(s^2+9)(90s^3+18s^2+40s+4)}$$

$$V(s) = \frac{A_1}{s-j3} + \frac{A_2 = A_1^*}{s+j3} + \frac{A_3}{s+0.05-j0.66} + \frac{A_4 = A_3^*}{s+0.05+j0.66} + \frac{A_5}{s+0.1}$$

To compute A_1 and A_3 , see lecture notes of week #5, Wed.:

complex

$$A_1 = (s-j3) \times V(s) \Big|_{s=j3} \cong 1.05 + j0.07$$

$$A_2 = A_1^* = 1.05 - j0.07$$

$$A_3 = (s+0.05-j0.66) \times V(s) \Big|_{s=-0.05+j0.66} \cong -0.05 - j0.02$$

$$A_4 = A_3^* = -0.05 + j0.02$$

Real: $A_5 = (s+0.1) \times V(s) \Big|_{s=-0.1} \cong 5.6 \times 10^{-5}$

- Hence:

$$V(s) = \frac{1.05+j0.07}{s-j3} + \frac{1.05-j0.07}{s+j3} - \frac{0.05+j0.02}{s+0.05-j0.66} - \frac{0.05-j0.02}{s+0.05+j0.66} + \frac{5.6 \times 10^{-5}}{s+0.1}$$

Finally, see lecture notes of week #5, Wed:

$$r(t) = \mathcal{L}^{-1} \{ V(s) \} =$$




$$= 5.6 \times 10^{-5} \cdot e^{-0.1t} \cdot u(t) +$$

$$2.1 \cdot \cos(3t + 3.91^\circ) \cdot u(t)$$

$$0.1 \cdot e^{-0.05t} \cdot \cos(0.66t + 157.9^\circ) \cdot u(t)$$

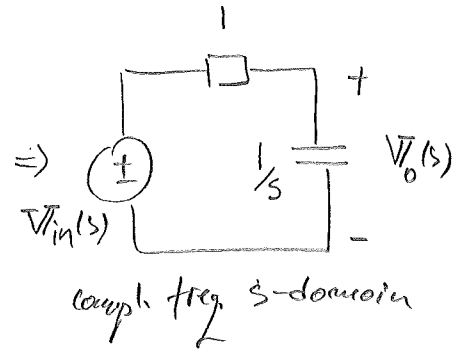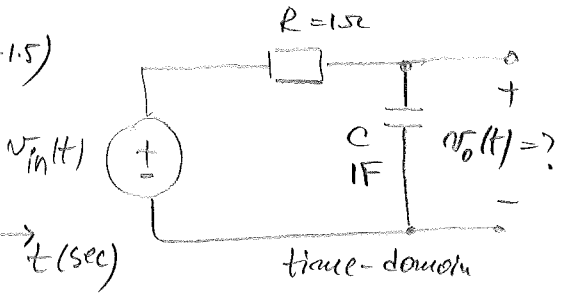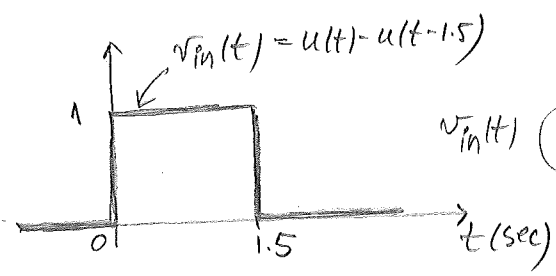Example 2:

Find the response of circuit to signal $v_{in}(t)$.



- observe that initial conditions are zero.
- Find network function ("output over input"): use voltage division: or transfer function

$$H(s) = \frac{V_o(s)}{V_{in}(s)} = \frac{1/s}{1 + 1/s} = \frac{1}{s+1}$$

- Therefore, the output or the response $V(s)$ can be computed as: (see lecture notes week #7, Wed):

$$V_o(s) = H(s) \cdot V_{in}(s) + \underbrace{V_{o,natural}(s)}_{=0 \text{ because there are no initial conditions.}}$$

$$\frac{1}{s+1} \cdot \frac{1}{s} - e^{-1.5s} \cdot \frac{1}{s} = \frac{1}{s} (1 - e^{-1.5s})$$

$$V_0(s) = \frac{1}{s+1} \times \frac{1}{s} (1 - e^{-1.5s}) = \frac{1}{s(s+1)} \cdot (1 - e^{-1.5s}) =$$

$$= \left[\frac{1}{s} - \frac{1}{s+1} \right] \cdot (1 - e^{-1.5s})$$

$$= \left(\frac{1}{s} - \frac{1}{s+1} \right) - \left(\frac{1}{s} - \frac{1}{s+1} \right) e^{-1.5s}$$

- Finally:

$$v_0(t) = \mathcal{L}^{-1} \left\{ V_0(s) \right\}$$

$$= \mathcal{L}^{-1} \left\{ \frac{1}{s} - \frac{1}{s+1} \right\} - \mathcal{L}^{-1} \left\{ \left(\frac{1}{s} - \frac{1}{s+1} \right) e^{-1.5s} \right\}$$

$$= (1 - e^{-t}) \cdot u(t) - [1 - e^{-(t-1.5)}] \cdot u(t-1.5)$$

