

Review for exam #3



Notes:

[Not given]

- I expect you to know that:

$$\tau = RC$$

$$\tau = \frac{L}{R}$$

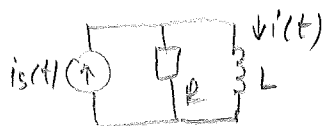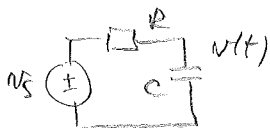

Given:

$$\tau \frac{dy(t)}{dt} + y(t) = x(t)$$

Constant forcing-function:

$$x(t) = X_s$$

$$y(t) = [y(0) - y(\infty)] e^{-\frac{t}{\tau}} + y(\infty)$$


$$x(t) = X_m \cos \omega t$$

$$y(t) = \left[y(0) - \frac{X_m}{1 + (\omega\tau)^2} \right] e^{-\frac{t}{\tau}} + \frac{X_m}{\sqrt{1 + (\omega\tau)^2}} \cos(\omega t - \tan^{-1} \omega\tau)$$

- You are expected to know that when $x(t) = 0$ the response (natural) is:

$$y(t) = y(0) e^{-\frac{t}{\tau}}$$


Example 1

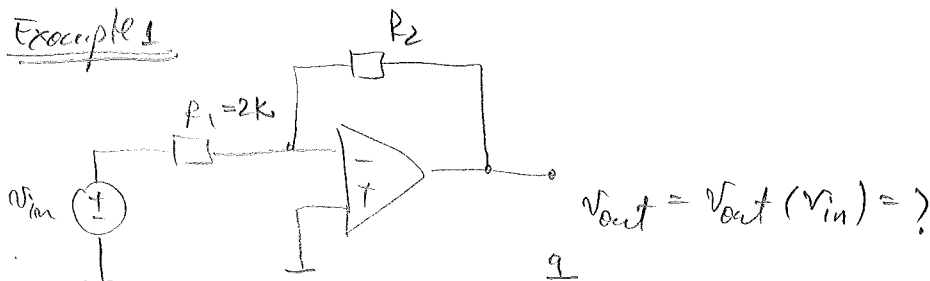

$$v_{out} = v_{out}(v_{in}) = ?$$

$$R_2 = ? \text{ such that } |gain| = 3$$


Example 2:

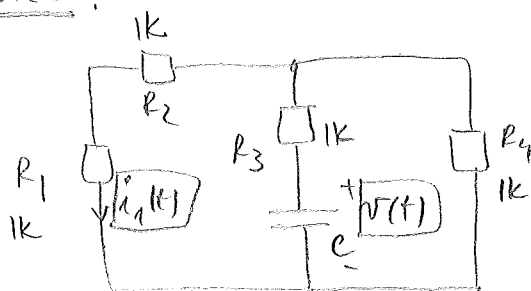


$$V_0 = v(0^-) = 15V; \quad v(t) = ?; \quad i_C(t) = ?$$

Example 3:

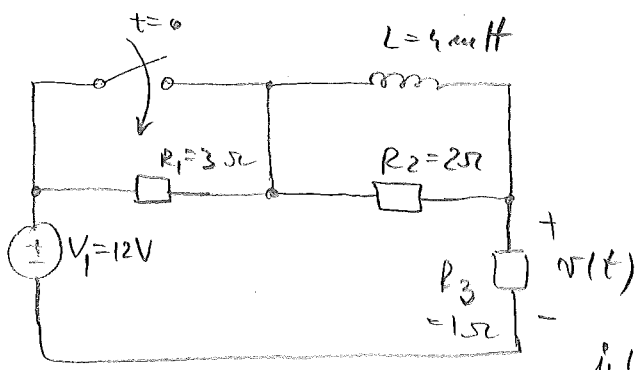(a) Sketch and label $v(t)$; (b) Find the instant when $v(t) = 10V$!



(a) $t < 0$

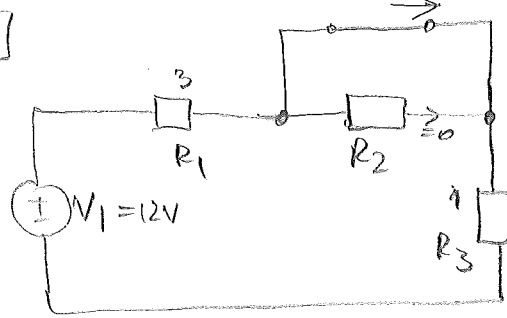


L is short in dc circuits let for long time!

$$v(0^-) = \frac{R_3}{R_1 + R_3} \cdot V_1 = \frac{1}{1+3} \cdot 12 = 3V$$

$$\text{Also: } i_L(0^-) = \frac{V_1}{R_1 + R_3} = \frac{12}{1+3} A = 3A = i_L(0^-)$$


(b) $t > 0$

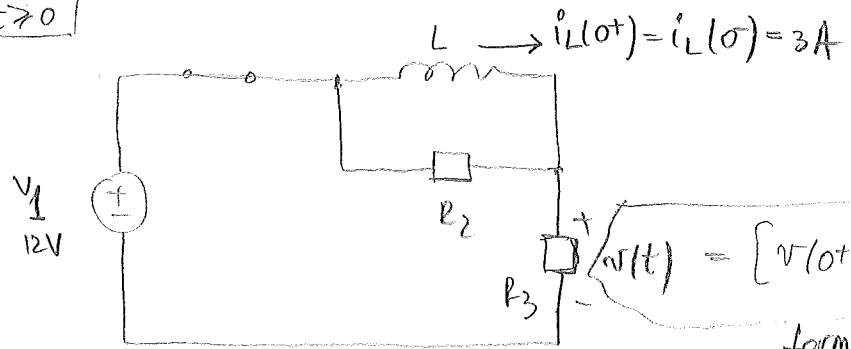


$$v(t) = [v(0^+) - v(\infty)] e^{-\frac{t}{\tau}} + v(\infty)$$

form expected.

► For $t = 0$

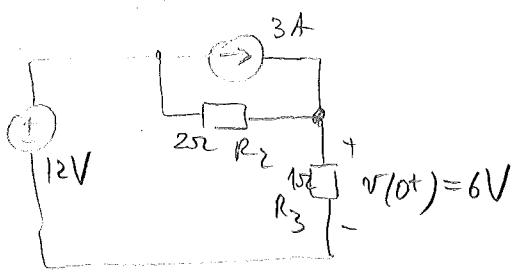

► For $t = \infty$

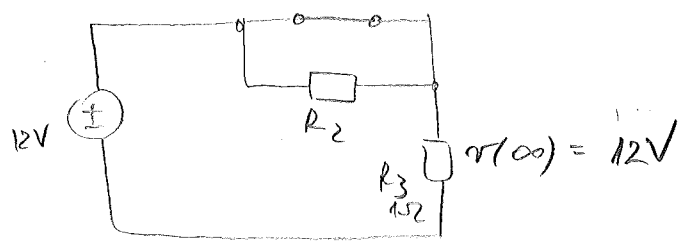


Use superposition:

$$\begin{aligned} v(0^+) &= \frac{R_3}{R_1 + R_3} \times 12V + (R_2 || R_3) \times 3A \\ &= \frac{1}{2+1} \times 12 + \frac{1 \cdot 2}{2+1} \times 3 \\ &= 6V \end{aligned}$$

we still need: $\tau = \frac{L}{R}$, $R \triangleq$ resistance "seen" by L at its terminals.


(3)

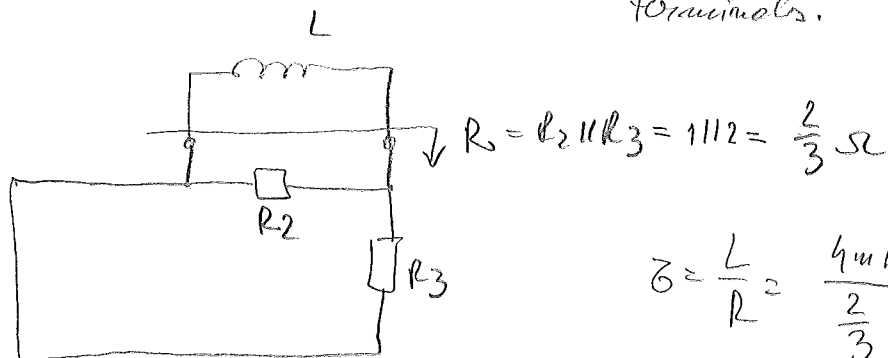


$$\tau = \frac{L}{R} = \frac{4 \text{ mH}}{\frac{2}{3}} = 6 \text{ ms}$$

Hence complete response/solution for $v(t)$:
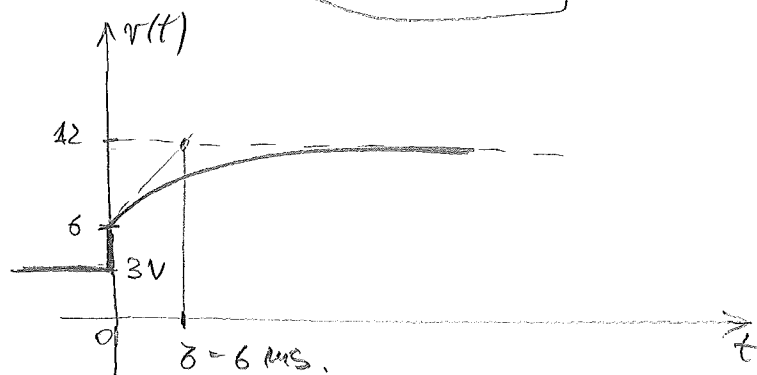
$$v(t) = [6 - 12] e^{-\frac{t}{6 \text{ ms}}} + 12 = 12 - 6 e^{-\frac{t}{6 \text{ ms}}} ; t \geq 0.$$



Verification: (skip this) (Method 2)

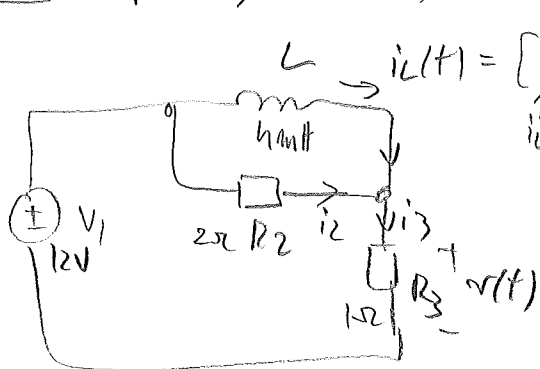

$$i_L(t) = [3 - 12] e^{-\frac{t}{6}} + 12 = 12 - 9 e^{-\frac{t}{6}}$$

$\uparrow$
 $i_L(0^+)$

$$\tau = \frac{L}{R}$$

$$v_L(t) = L \frac{di}{dt} = 4 \cdot \frac{1}{6} \cdot 9 e^{-\frac{t}{6}} = \frac{2}{3} \cdot 9 e^{-\frac{t}{6}} = 6 e^{-\frac{t}{6}}$$

$$i_2 = \frac{v_L(t)}{R_2} = 3 e^{-\frac{t}{6}}$$

$$i_L(t) + i_2(t) = i_3(t)$$


$$12 - 9 e^{-\frac{t}{6}} + 3 e^{-\frac{t}{6}} = i_3(t) = 12 - 6 e^{-\frac{t}{6}}$$

$$v(t) = R_3 \cdot i_3(t) = 12 - 6 e^{-\frac{t}{6}} ; t \geq 0$$


same result!

Example (9)

Sketch the voltage $v(t)$

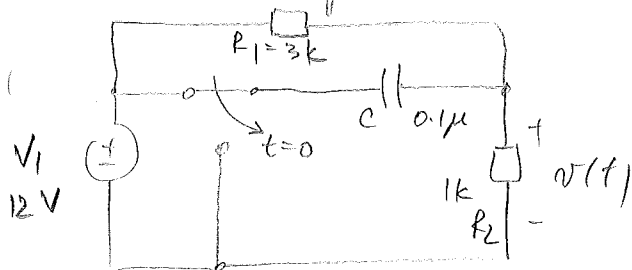

(1) $t < 0$

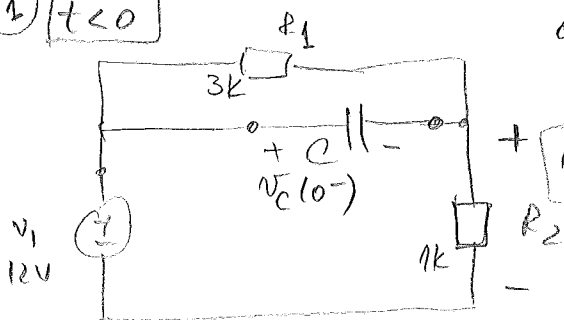


after very long transients have died out, this is a dc circuit with C an open circuit!

$$v(0^-) = \frac{R_2}{R_1 + R_2} V_1 = \frac{1}{3+1} \times 12V = 3V$$


By KVL: $v_C(0^-) = V_1 - v(0^-) = (12-3)V = 9V$

(2) $t \geq 0$

(a) $t = 0^+$ $v(0^+) = ?$

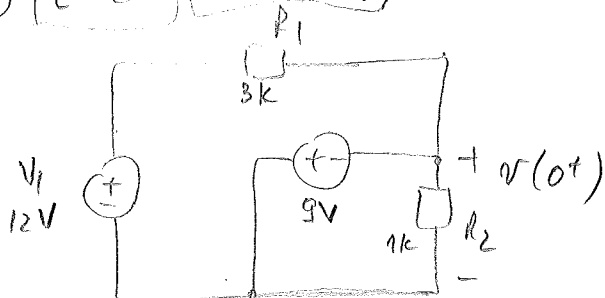


By KVL we have $v(0^+) = -9V$

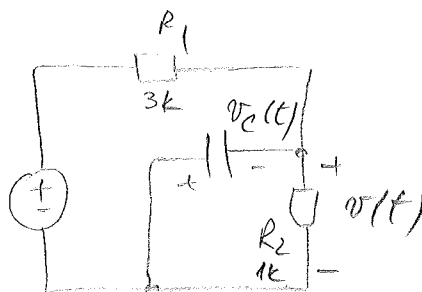

We expect:

$$v(t) = [v(0^+) - v(\infty)] e^{-\frac{t}{\tau}} + v(\infty)$$

(b) $t = \infty$ $v(\infty) = ?$

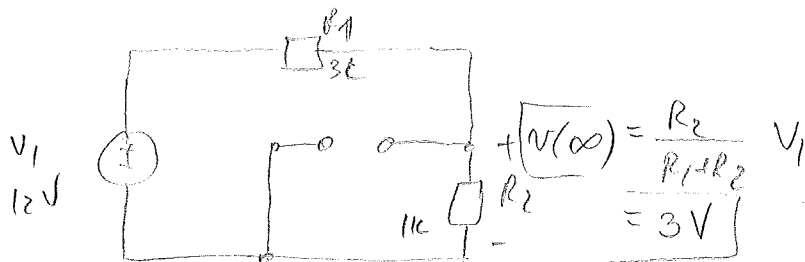


$$v(\infty) = \frac{R_2}{R_1 + R_2} V_1 = \frac{1}{3+1} \times 12V = 3V$$

hence:

$$v(t) = [-9 - 3] e^{-\frac{t}{\tau}} + 3 = 3 - 12 e^{-\frac{t}{\tau}} = v(t) \quad t \geq 0$$

(c) $\tau = RC = \frac{3}{4}k \times 0.1\mu F = \frac{0.3}{4}ms$

↑
resistance seen by C at its terminals!

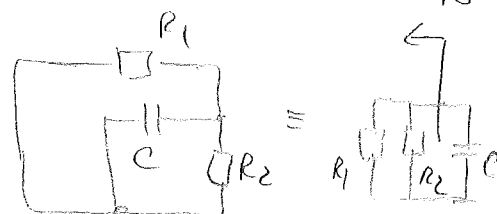

$$R = R_1 || R_2 = 1 || 3 = \frac{1 \times 3}{1+3} = \frac{3}{4}k$$

